

IES / GATE

Electrical Engineering

VOLUME-IV

Analog & Digital Electronics


Contents

Analog

1-259

Digital Electronics

260-461

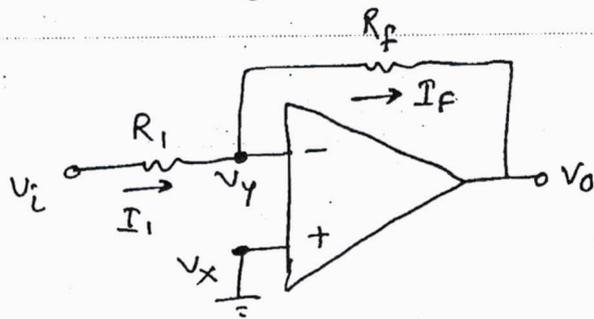Analog
Electronics - (2)Topic - 43op Amp Applications- A. RAJKUMARLinear applicationsAmplifiers① Inverting Amplifier:Virtual ground Theory

$$V_y = V_x$$

$$I_i = I_f$$

$$\frac{V_i - V_y}{R_i} = \frac{V_y - V_o}{R_f}$$

$$\frac{V_i - 0}{R_i} = \frac{0 - V_o}{R_f}$$

Then
$$\frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

(closed loop gain A_{CL})practical error

$$V_x \neq V_y$$

$$V_o = A_d V_d$$

$$= A_d (V_x - V_y)$$

$$= A_d (0 - V_y)$$

$$= -A_d V_y$$

Then
$$V_y = -V_o / A_d$$

$$I_i = I_f$$

$$\frac{V_i - V_y}{R_i} = \frac{V_y - V_o}{R_f}$$

$$V_y \left[\frac{1}{R_f} + \frac{1}{R_1} \right] = \frac{V_i}{R_1} + \frac{V_o}{R_f}$$

$$V_y \left[\frac{R_1 + R_f}{R_1 R_f} \right] - \frac{V_o}{R_f} = \frac{V_i}{R_1}$$

$$-\frac{V_o}{A_d} \left[\frac{R_1 + R_f}{R_1 R_f} \right] - \frac{V_o}{R_f} = \frac{V_i}{R_1}$$

$$-\frac{V_o}{R_f} \left[\left[1 + \frac{R_f}{R_1} \right] \frac{1}{A_d} + 1 \right] = \frac{V_i}{R_1}$$





$$\frac{V_o}{V_i} = \frac{-R_f/R_1}{1 + \frac{1}{A_d} \left[1 + \frac{R_f}{R_1} \right]}$$

practical error


conclusions

- (1) The voltage gain is low
 - (2) The input impedance is low
- } drawbacks

Example problems

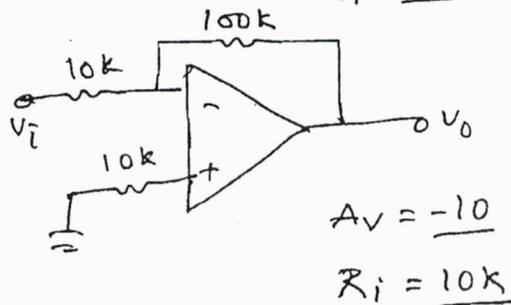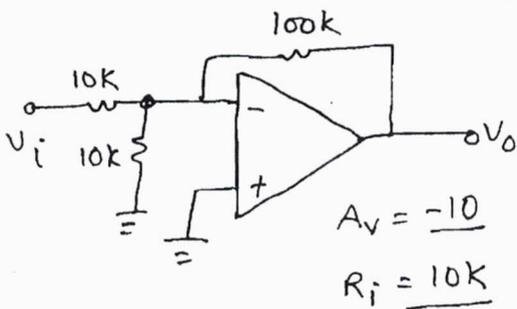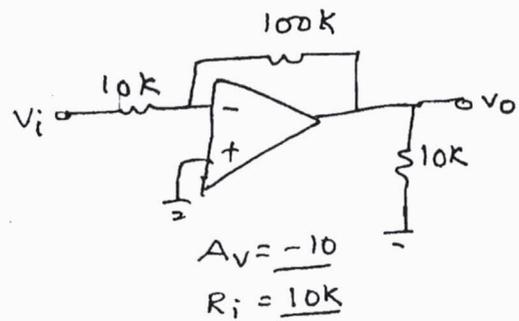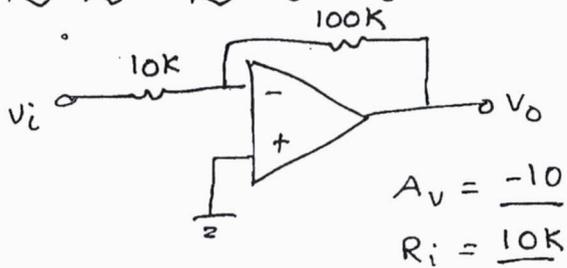

② Non-Inverting Amplifier

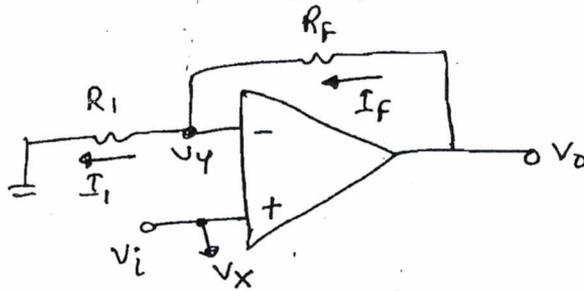

Virtual ground theory

$$V_x = V_y = V_i$$

$$I_f = I_i$$

$$\frac{V_o - V_y}{R_f} = \frac{V_y - 0}{R_i}$$

Then
$$\frac{V_o - V_i}{R_f} = \frac{V_i - 0}{R_i}$$

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$$

practical error

$$V_x \neq V_y$$

$$\frac{V_o}{V_i} = \frac{\left[1 + \frac{R_f}{R_i}\right]}{1 + \frac{1}{A_d} \left[1 + \frac{R_f}{R_i}\right]}$$


Input impedance

$$Z_i = \frac{V_i}{I_i} = \frac{V_i}{0} = \infty \text{ (high impedance)}$$

conclusions

- ① The voltage gain is low (drawback)
- ② The input impedance is high (advantage)

③ voltage buffers

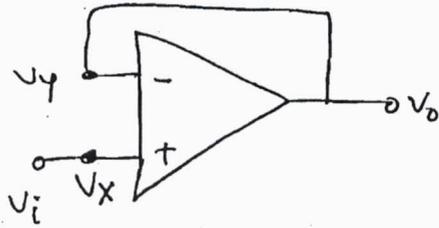

virtual ground

$$V_x = V_y$$

here $V_x = V_i$

$$V_y = V_o$$

$$\therefore V_i = V_o$$

The voltage gain = $\frac{V_o}{V_i} = 1$ (unity gain)


practical errors

$$V_o = A_d V_d = A_d (V_i - V_o)$$

$$V_o (1 + A_d) = A_d V_i$$

$$\boxed{\frac{V_o}{V_i} = \frac{A_d}{1 + A_d}}$$

④ phase shifter

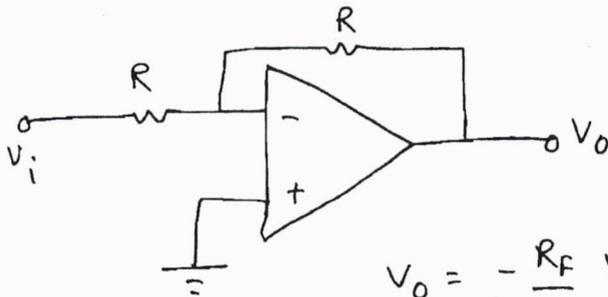


$$V_o = -\frac{R_f}{R_i} V_i \quad (\text{inverting Amplifier})$$

$$= -\frac{R}{R} V_i$$

$$\boxed{V_o = -V_i}$$

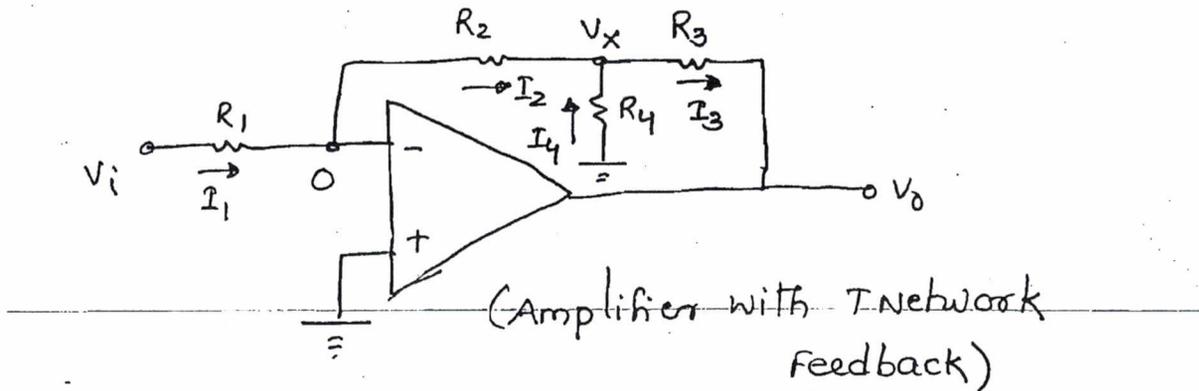⑤ Improvement of voltage gain in Inverting Amplifier



$$V_x = -\frac{R_2}{R_1} V_i$$

KCL @ T network

$$I_2 + I_4 = I_3$$

$$\frac{0 - V_x}{R_2} + \frac{0 - V_x}{R_4} = \frac{V_x - V_o}{R_3}$$

$$\frac{V_o}{R_3} = V_x \left[\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right]$$


$$\frac{V_o}{R_3} = -\frac{R_2}{R_1} V_i \left[\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right]$$

$$\frac{V_o}{V_i} = -\frac{R_2 R_3}{R_1} \left[\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right]$$

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} \left[1 + \frac{R_3}{R_2} + \frac{R_3}{R_4} \right]$$

(6) Differential Amplifier


model-1

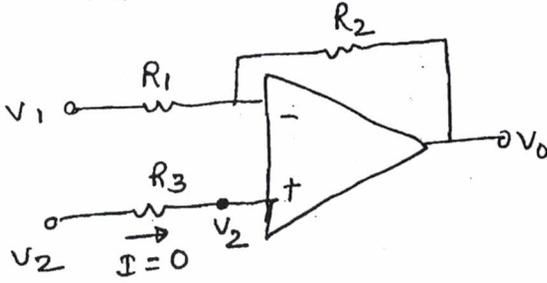

using Superposition Theorem

$$V_0 = -\frac{R_2}{R_1} V_1 + \left(1 + \frac{R_2}{R_1}\right) V_2$$


model-2

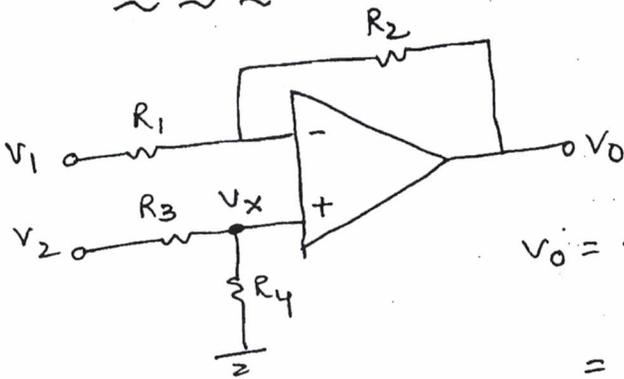

$$V_0 = -\frac{R_2}{R_1} V_1 + \left(1 + \frac{R_2}{R_1}\right) V_x$$

$$= -\frac{R_2}{R_1} V_1 + \left(1 + \frac{R_2}{R_1}\right) V_2 \times \frac{R_4}{R_3 + R_4}$$

model-3

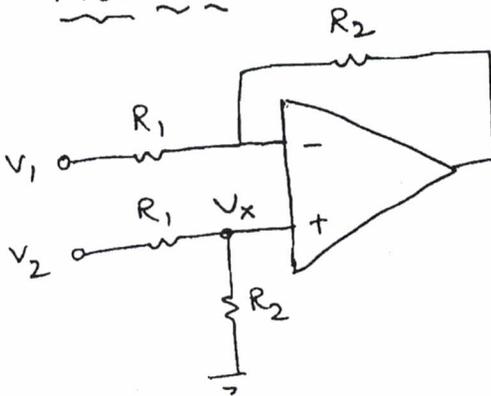

$$V_0 = -\frac{R_2}{R_1} V_1 + \left(1 + \frac{R_2}{R_1}\right) V_x$$

$$= -\frac{R_2}{R_1} V_1 + \left(1 + \frac{R_2}{R_1}\right) V_2 \times \frac{R_2}{R_1 + R_2}$$

$$= -\frac{R_2}{R_1} V_1 + \frac{R_1 + R_2}{R_1} V_2 \times \frac{R_2}{R_1 + R_2}$$

$$V_0 = \frac{R_2}{R_1} (V_2 - V_1)$$


CMRR is maintained.

⑦ Instrumentational Amplifier

CMRR (common mode Rejection ratio)

$$CMRR = \frac{A_d}{A_c}$$

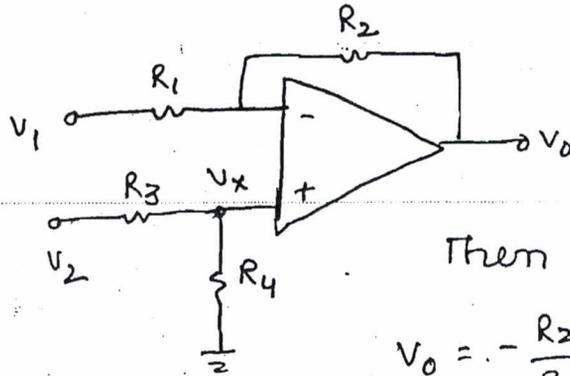where $A_d \rightarrow$ differential gain
 $A_c \rightarrow$ common mode gain



Then

$$\begin{aligned} V_0 &= -\frac{R_2}{R_1} V_1 + \left[1 + \frac{R_2}{R_1}\right] V_x \\ &= -\frac{R_2}{R_1} V_1 + \left[1 + \frac{R_2}{R_1}\right] \frac{R_4}{R_3 + R_4} V_2 \end{aligned}$$

$$V_0 = A_1 V_1 + A_2 V_2$$

$$\left. \begin{aligned} V_d &= V_2 - V_1 \\ V_c &= \frac{V_1 + V_2}{2} \end{aligned} \right\}$$

where $V_d \rightarrow$ differential voltage

$V_c \rightarrow$ common mode voltage

$$\left. \begin{aligned} V_2 &= \frac{V_d}{2} + V_c \\ V_1 &= -\frac{V_d}{2} + V_c \end{aligned} \right\}$$

$$\begin{aligned} V_0 &= A_1 \left[-\frac{V_d}{2} + V_c \right] + A_2 \left[\frac{V_d}{2} + V_c \right] \\ &= \underbrace{\left[\frac{A_2 - A_1}{2} \right]}_{A_d} V_d + \underbrace{(A_1 + A_2)}_{A_c} V_c \end{aligned}$$

where

$$A_d = \frac{A_2 - A_1}{2}$$

$$A_c = A_1 + A_2$$

$$CMRR = \frac{A_d}{A_c}$$

output voltage V_o error

$$V_o = A_d V_d + A_c V_c$$


$$= A_d V_d \left[1 + \frac{A_c}{A_d} \frac{V_c}{V_d} \right]$$

$$V_o = A_d V_d \left[1 + \frac{1}{CMRR} \times \frac{V_c}{V_d} \right]$$

practical error

$$= \frac{1}{CMRR} \frac{V_c}{V_d}$$

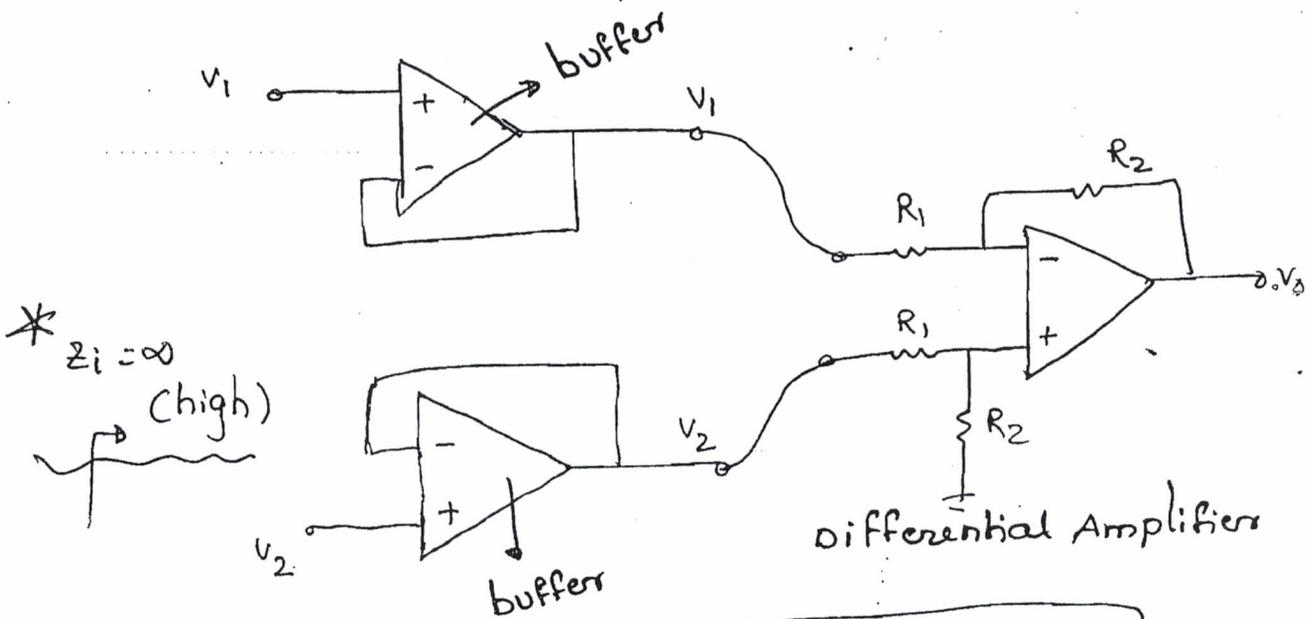Instrumentational Amplifier using 3 opamps




$$V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

* CMRR is maintained

* voltage gain is low

modified circuit

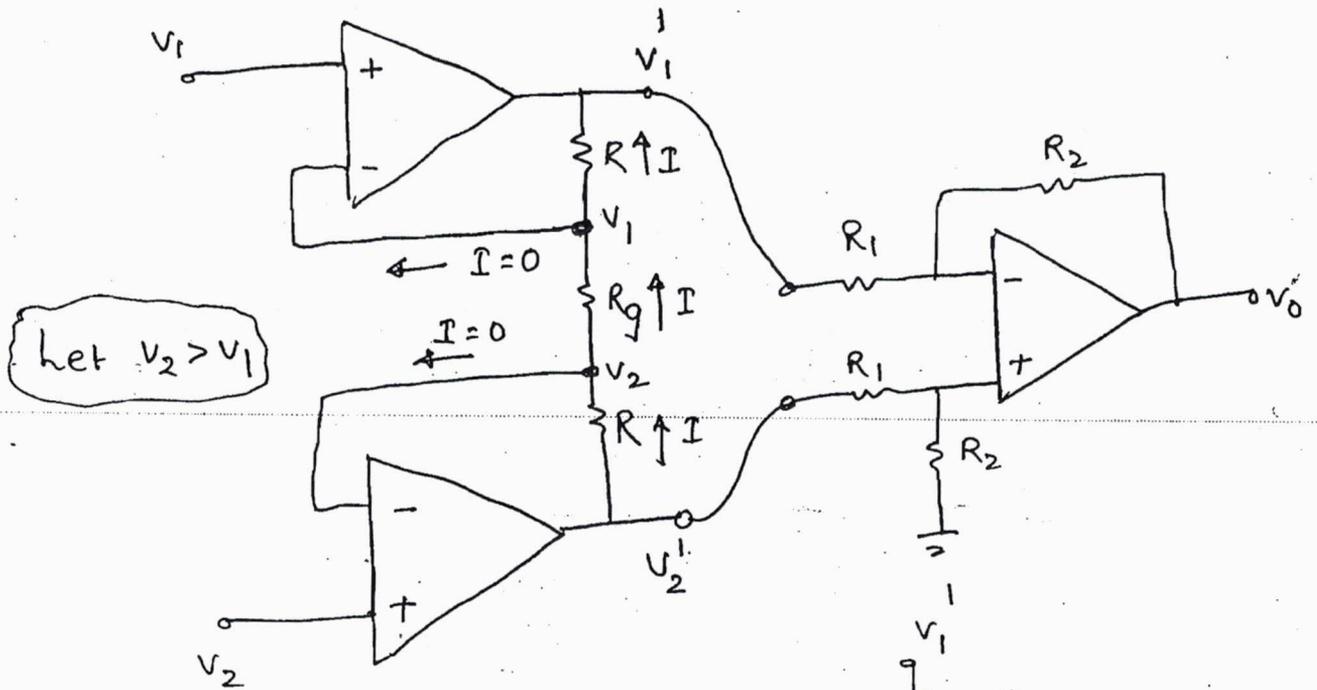

let $V_2 > V_1$

$$V_0 = \frac{R_2}{R_1} (V_2' - V_1')$$

$$V_1' = -IR + V_1$$

$$V_2' = IR + V_2$$


$$V_0 = \frac{R_2}{R_1} (IR + V_2 - (-IR + V_1))$$

$$= \frac{R_2}{R_1} [IR + V_2 + IR - V_1]$$

$$= \frac{R_2}{R_1} [2IR + V_2 - V_1]$$

$$= \frac{R_2}{R_1} \left[(V_2 - V_1) + 2 \cdot (V_2 - V_1) \cdot \frac{R}{R_g} \right]$$

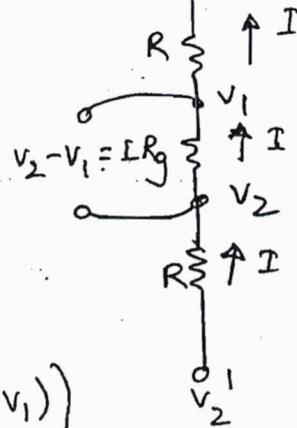
$$V_0 = \frac{R_2}{R_1} (V_2 - V_1) \left[1 + \frac{2R}{R_g} \right]$$



$$\frac{V_o}{V_2 - V_1} = \frac{R_2}{R_1} \left[1 + \frac{2R}{R_g} \right]$$

- voltage gain is high
 - Input impedance is high
 - CMRR is maintained
- } advantages

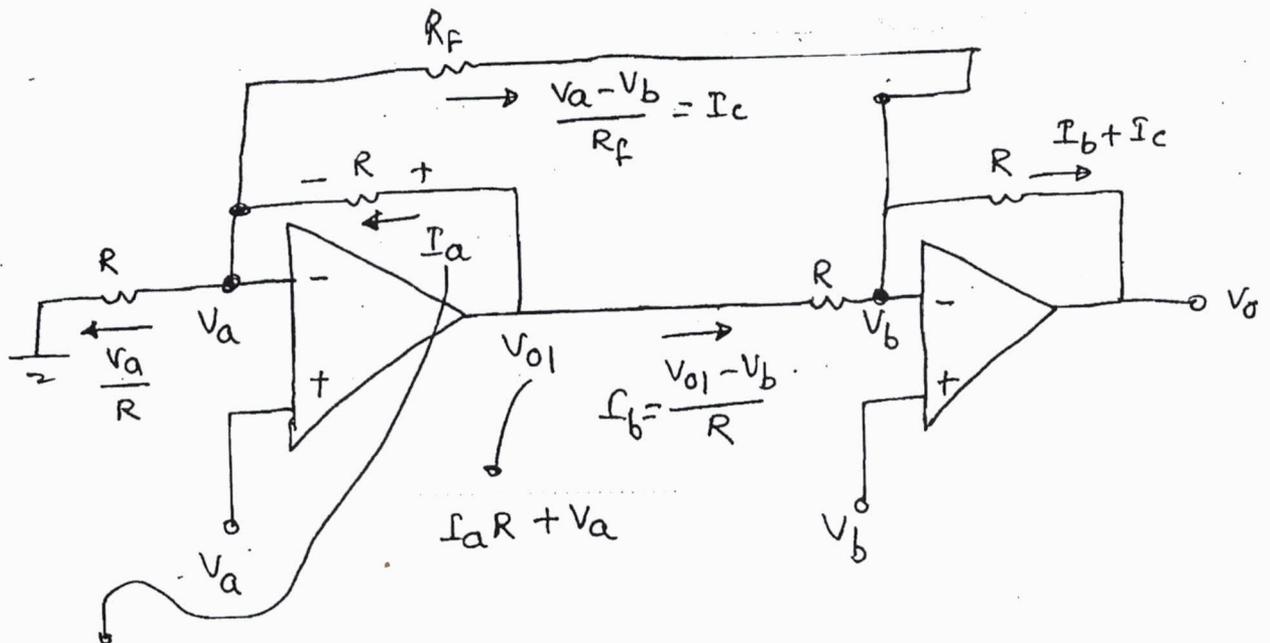Instrumentational Amplifier using two opAmps



$$I_a = \frac{V_a}{R} + \frac{V_a - V_b}{R_f}$$

After Simplification


$$V_o = 2(V_b - V_a) \left(1 + \frac{R}{R_f} \right)$$

$$\frac{V_o}{V_b - V_a} = 2 \left[1 + \frac{R}{R_f} \right]$$

mathematical operations

① Adder

Inverting Adder

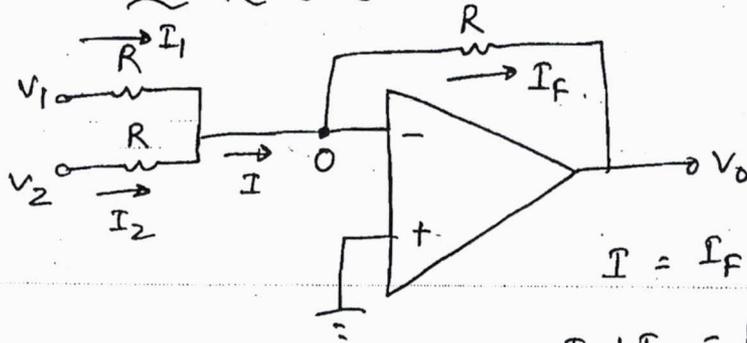

$$I = I_f$$


$$I_1 + I_2 = I_f$$

$$\frac{V_1}{R} + \frac{V_2}{R} = \frac{0 - V_0}{R}$$

$$\frac{1}{R} (V_1 + V_2) = -\frac{V_0}{R}$$

$$V_0 = -(V_1 + V_2)$$

Non Inverting adder

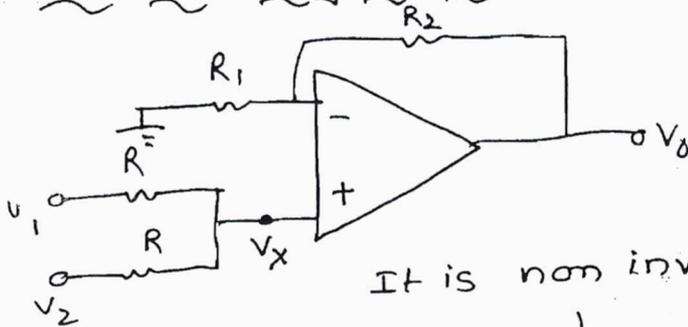

It is non inverting Amplifier with input V_x where $V_x = V_1 \times \frac{R}{R+R} + V_2 \times \frac{R}{R+R}$

$$= \frac{V_1 + V_2}{2}$$

$$V_0 = \left[1 + \frac{R_2}{R_1} \right] V_x$$

$$= \left[1 + \frac{R_2}{R_1} \right] \frac{V_1 + V_2}{2}$$


Suppose

$R_1 = R_2 = R$ Then

$$V_0 = \cancel{2} \cdot \frac{V_1 + V_2}{\cancel{2}}$$

$$V_0 = V_1 + V_2$$

② Subtractor

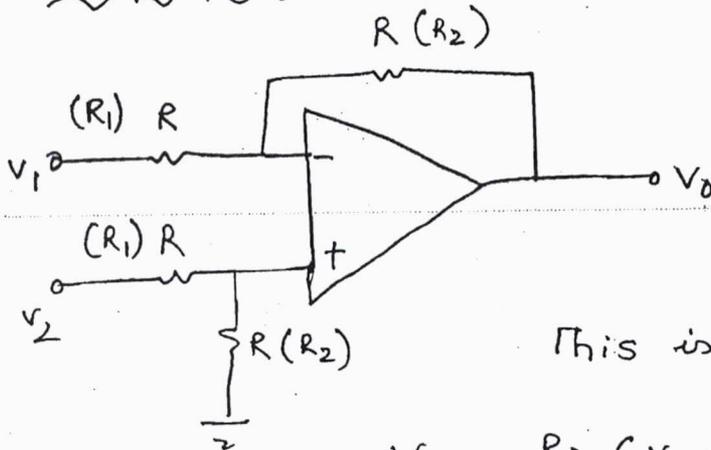


This is differential Amplifier

$$V_0 = \frac{R_2}{R_1} (V_2 - V_1)$$

now $R_1 = R_2 = R$

Then $V_0 = V_2 - V_1$

③ Logarithmic amplifier

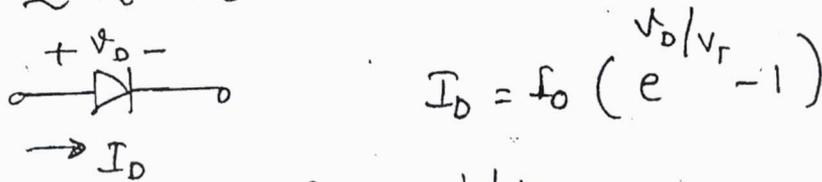


$$I_D = I_0 \left(e^{\frac{V_D}{V_T}} - 1 \right)$$

In forward bias


$$I_D = I_0 e^{\frac{V_D}{V_T}}$$

$$V_D = V_T \ln \left(\frac{I_D}{I_0} \right)$$

Logarithmic

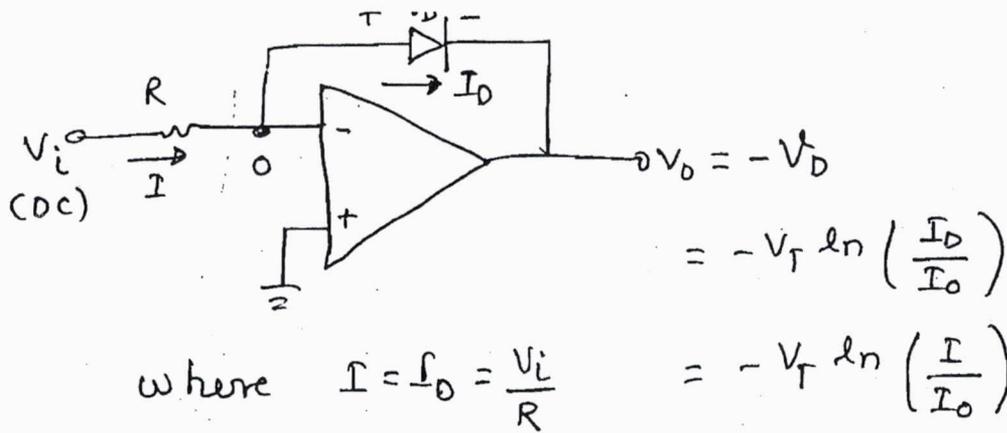
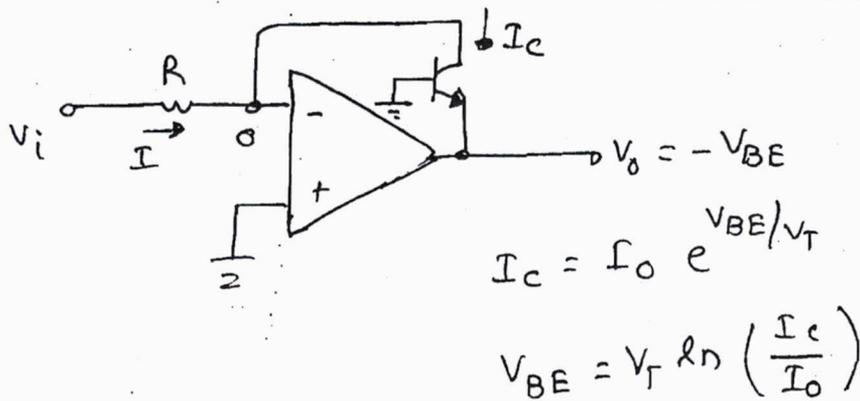
$$V_o = -V_T \ln \left(\frac{V_i}{I_0 R} \right)$$




$$V_o = -V_T \ln \left(\frac{V_i}{I_0 R} \right)$$

Note:

In discrete electronics diode is used as a logarithmic operation

In integrated electronics BJT is used as a logarithmic operation.

(4) Analog Amplifier

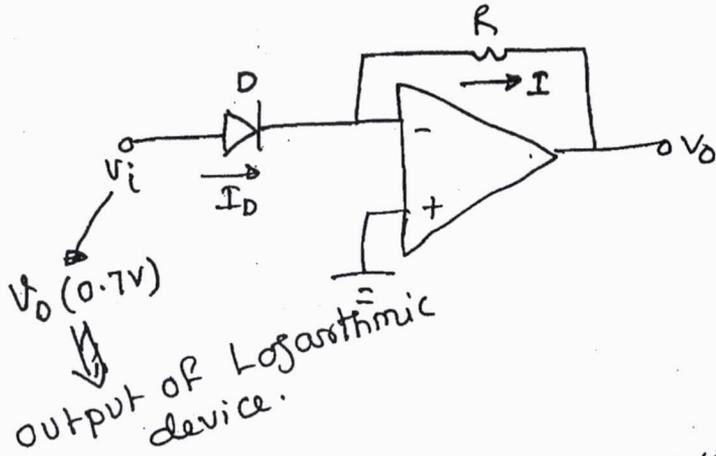

$$I_D = I_0 e^{V_D/V_T}$$

where $V_D = V_i$


$$I_D = I_0 e^{V_i/V_T}$$

where $I_D = I$


$$I = I_0 e^{V_i/V_T}$$

$$\frac{0 - V_o}{R} = I_0 e^{V_i/V_T}$$

$$V_o = -I_0 R e^{V_i/V_T}$$

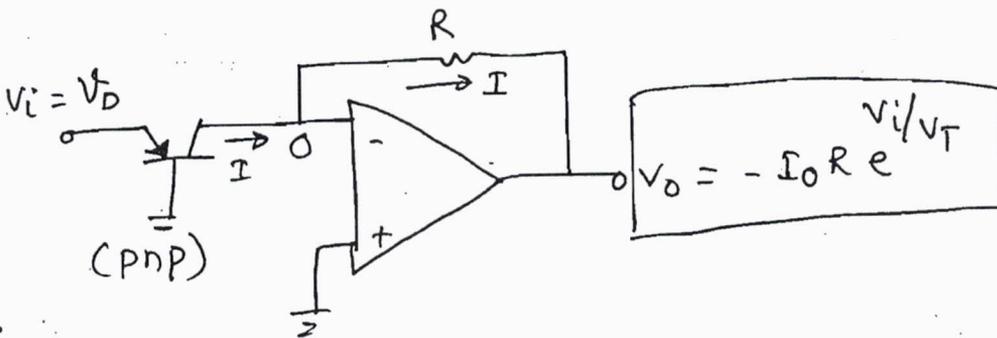


$$V_o = -I_0 R e^{V_i/V_T}$$

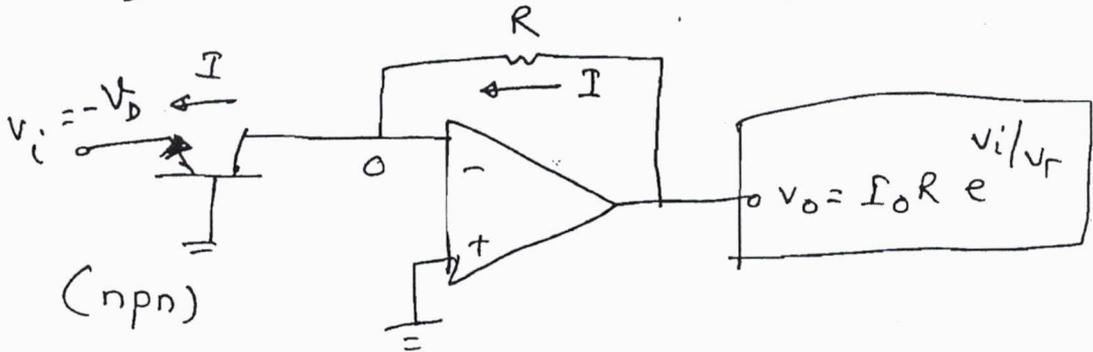

$$V_o = I_0 R e^{V_i/V_T}$$


⑤ Analog multipliers (modulator)

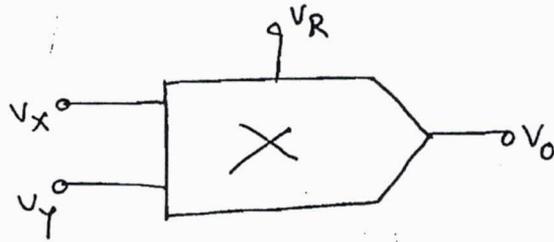

$$V_o = \frac{V_x \cdot V_y}{V_R}$$

where $V_R \rightarrow$ Reference voltage
(Typically 10V)

⑥ Analog divider (Demodulator)

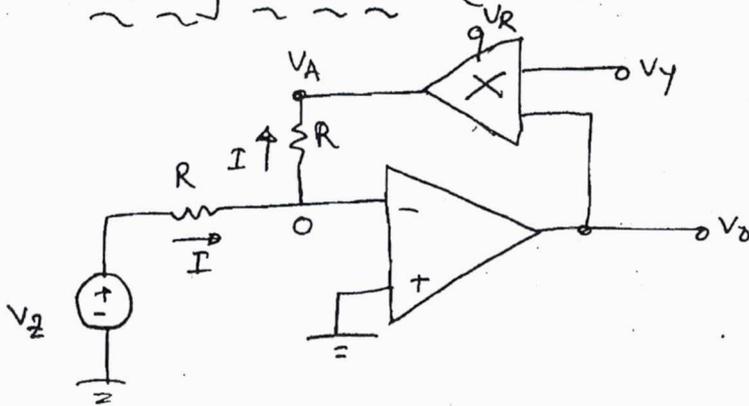

$$\frac{V_2 - 0}{R} = \frac{0 - V_A}{R}$$


$$V_2 = -V_A$$

$$= -\frac{V_y V_o}{V_R}$$

$$\left[V_A = \frac{V_y \cdot V_o}{V_R} \right]$$

$$V_o = -V_R \cdot \left[\frac{V_2}{V_y} \right]$$

⑦ Square root amplifier

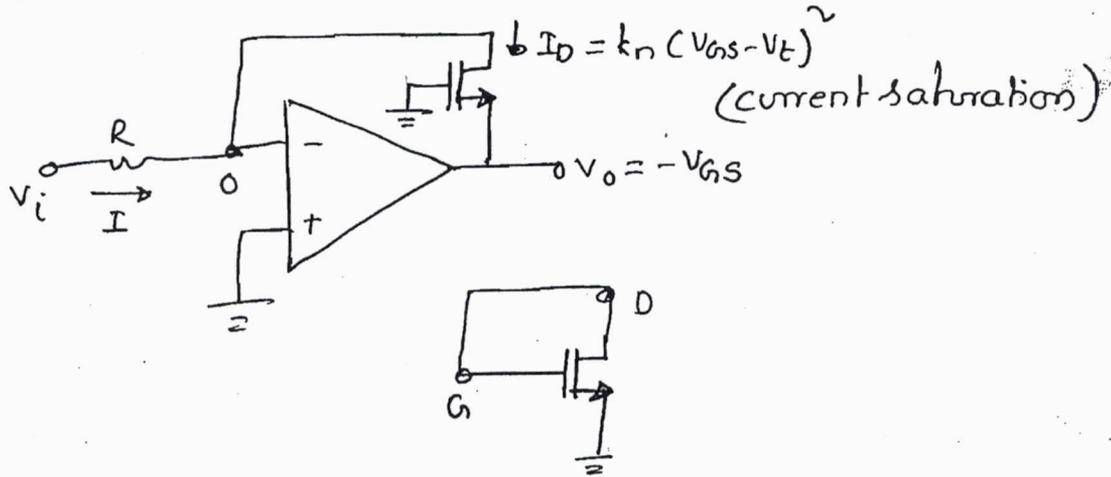

Diode connected MOSFET will always work in current saturation.

$$I = I_D = \frac{V_i - 0}{R} = \frac{V_i}{R}$$

$$V_o = -V_{GS}$$

$$I_D = k_n (V_{GS} - V_T)^2$$

$$\frac{V_i}{R} = k_n (-V_o - V_T)^2$$

$$V_o = -\sqrt{\frac{V_i}{Rk_n}} - V_T$$

⑧ Integrator:

