



# CSIR-NET

Council of Scientific & Industrial Research

## PHYSICAL SCIENCE

VOLUME - IV

ELECTRONICS




## ELECTRONICS

1.	Network Analysis	1
2.	Norton's Law	11
3.	Semiconductor Physics	16
4.	PN Junction Diode	34
5.	AC Application	42
6.	Zener Diode as a Voltage Regulator	53
7.	Bipolar Junction Transistor	62
8.	Bios Stabilization	79
9.	Opto Electronics	89
10.	Light Emited Diode (LED)	97
11.	Operational Amplifier	100
12.	Compartor	115
13.	Oscillator	125
14.	Digital Electronics	130
15.	Flip flop & Their application	144
16.	Curve Fitting	160
17.	Transducers	166
18.	Types of Junction Detectors	189
19.	Noise	196
20.	Grounding	199
21.	Modulation Technics	204
22.	High Frequency Devices	208

## NETWORK ANALYSIS

i) Kirchoff's Voltage Law:-

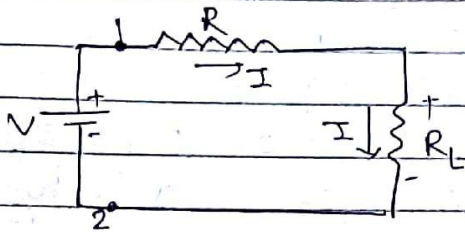

$$V - IR - IR_L = 0$$


$$I = \frac{V}{R + R_L} = \frac{V}{R_{eq,12}} \quad (R_{eq} = R + R_L)$$

→ Sum of the voltage in any closed loop must be zero. Considering same sign convention.

Voltage drop across R  $V_R = IR = \frac{VR}{R + R_L}$

$V_{R_L} = IR_L = \frac{VR_L}{R + R_L}$  } voltage division Rule.

Ex-

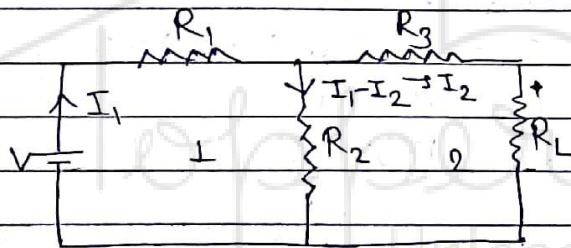

loop 1  $V - I_1 R_1 - (I_1 - I_2) R_2 = 0$

loop 2  $(R_3 + R_L) I_2 - (I_1 - I_2) R_2 = 0$

$$V = I_1 (R_1 + R_2) - I_2 R_2$$

$$0 = -R_2 I_1 + (R_3 + R_L + R_2) I_2$$

$$I_2 = \frac{R_2 I_1}{R_3 + R_L + R_2}$$


$$V = I_1 (R_1 + R_2) - \frac{I_1 R_2^2}{R_3 + R_L + R_2}$$

$$= \left[ \frac{(R_1 + R_2)(R_3 + R_L + R_2) - R_2^2}{(R_3 + R_L + R_2)} \right] I_1$$

$$I_1 = \frac{V (R_2 + R_3 + R_L)}{R_1 R_3 + R_1 R_2 + R_2 R_3 + R_1 R_L + R_2 R_L}$$

$$I_2 = \frac{V R_2}{R_1 (R_3 + R_2 + R_L) + R_2 (R_3 + R_L)}$$

eg.

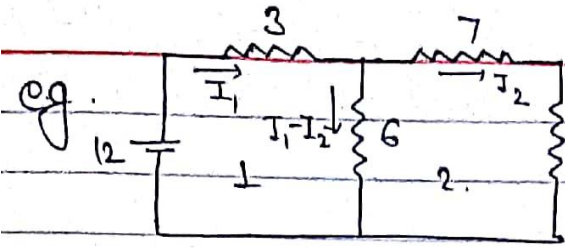

$$12 - 3I_1 - 6(I_1 - I_2) = 0$$

$$9I_1 - 6I_2 = 12$$

$$3I_1 - 2I_2 = 4$$

(ii)  $14I_2 - 6(I_1 - I_2) = 0$


$$8I_1 + 6I_2 = 0 \quad 6I_1 = -8I_2$$

$$I_1 = -\frac{4}{3}I_2 \quad I_1 = \frac{10}{3}I_2$$

$$3\left(-\frac{4}{3}I_2\right) - 2I_2 = 4 \Rightarrow -4I_2 - 2I_2 = 4$$

$$I_2 = -\frac{16}{17} \quad 10I_2 - 2I_2 = 4$$

$$8I_2 = 4$$
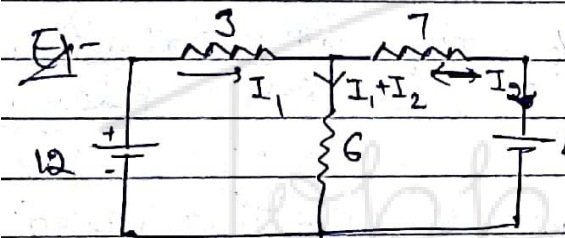
$$I_1 = \frac{5}{3} \text{ amp} \quad I_2 = \frac{1}{2} \text{ amp}$$


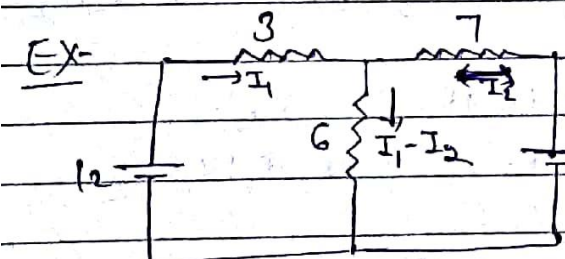
$$12 - 3I_1 - 6(I_1 + I_2) = 0$$

$$6 - 7I_2 - 6(I_1 + I_2) = 0$$

$$9I_1 + 6I_2 = 12$$

$$6I_1 + 13I_2 = 6$$

Ex-




$$12 - 3I_1 - 6(I_1 - I_2) = 0$$

$$6 + 7I_2 - 6(I_1 - I_2) = 0$$

$$9I_1 + 6I_2 = 12$$


Ex-

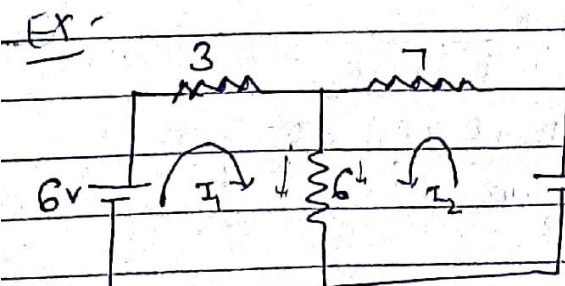

$$6 - 9I_1 - 6I_2 = 0$$

$$12 - 13I_2 - 6I_1 = 0$$

## Current division Rule:

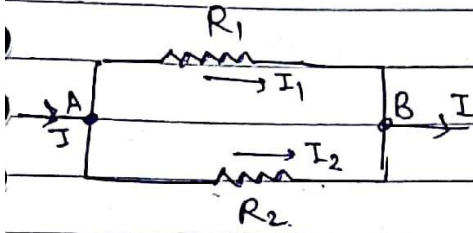

$$V_{AB} = I_1 R_1 = I_2 R_2$$


$$I = I_1 + I_2 = IR$$

$$I_2 = \frac{I R_1}{R_1 + R_2}$$

$$I_1 = \frac{I R_2}{R_1 + R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Ex-

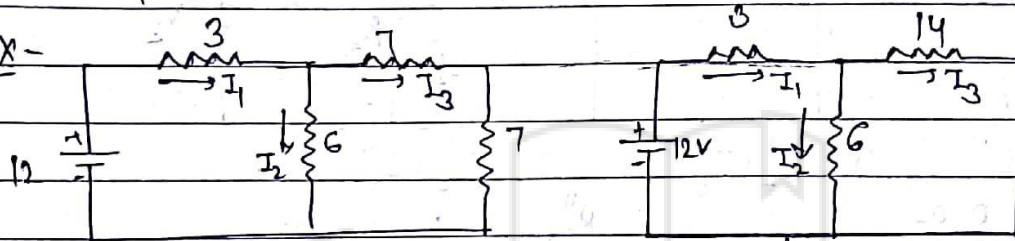


$$R_{eq} = 3 + \frac{6 \times 7}{6 + 7} = 3 + 4.2 = 7.2 \Omega$$

$$I_1 = \frac{12}{7.2} \times \frac{10}{6} = \frac{5}{3} \text{ amp.}$$

$$I_2 = \frac{6}{6+7} \times \frac{14 \times 5}{3} = \frac{7}{6} \text{ amp} \quad I_3 = \frac{6}{6+14} \times \frac{5}{3} = \frac{1}{2} \text{ amp}$$

Ex-

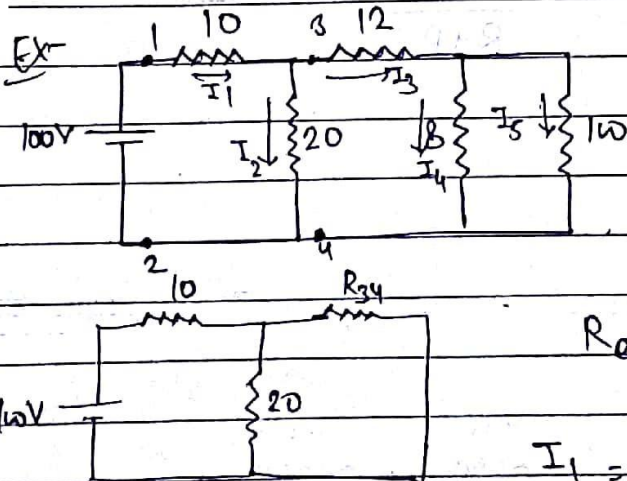

$$R_{34} = 12 + \frac{8 \times 10}{8 + 10} = 12 + \frac{80}{18} = 12 + 7.5 = 19.5$$

$$R_{eq} = 10 + \frac{20 \times 19.5}{20 + 19.5} = 20 \Omega$$

$$I_1 = \frac{100}{20} = 5 \text{ A}$$



$$I_2 = \frac{100 \times 5 \times 19.5}{20 + 19.5}$$

$$I_3 = \frac{20 \times I_1}{20 + 19.5}$$

$$I_4 = \frac{I_3 \times 10}{8 + 10}$$

$$I_5 = \frac{8 \times I_3}{108}$$

## Superposition Theorem :-

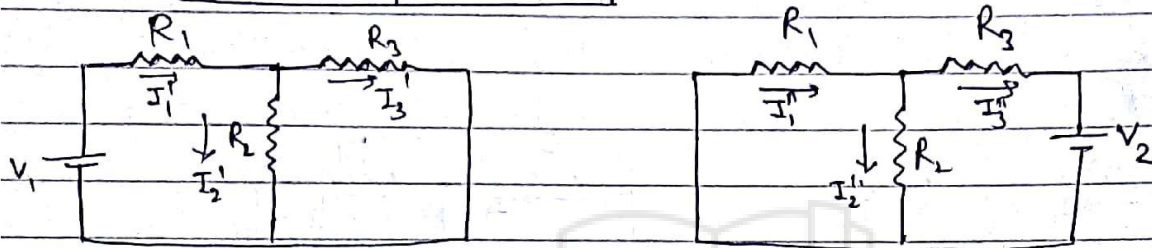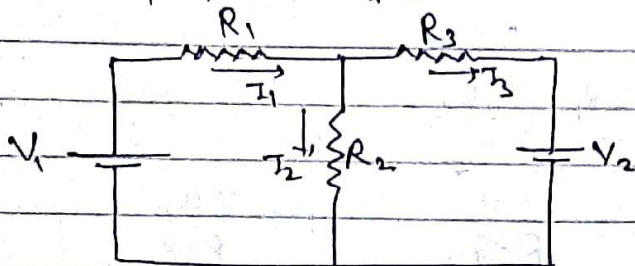

$$I_1 = I_1' + I_1'' \quad I_2 = I_2' + I_2'' \quad I_3 = I_3' + I_3''$$

$$R_{eq}' = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

$$R_{eq}'' = R_3 + \frac{R R_2}{R + R_2}$$

$$I_1' = \frac{V_1}{R_{eq}'}$$

$$I_3'' = \frac{V_2}{R_{eq}''}$$



$$I_2' = \frac{R_3 I_1'}{R_2 + R_3}$$

$$I_2'' = \frac{I_3'' R_1}{R_1 + R_2}$$

$$I_3' = \frac{R_2 I_1'}{R_2 + R_3}$$

$$I_1'' = \frac{I_3'' R_2}{R_1 + R_2}$$

EX -

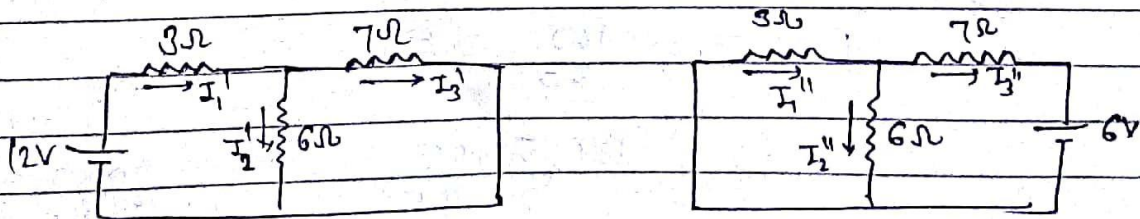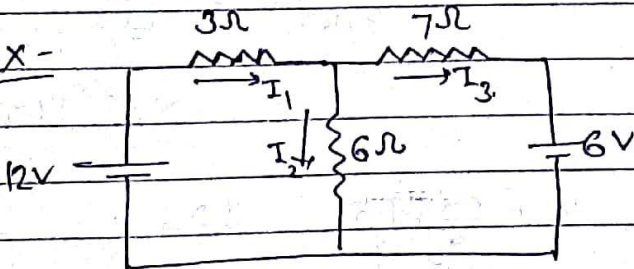




$$I_1 = I_1' + I_1'' \quad I_2 = I_2' + I_2'' \quad I_3 = I_3' + I_3''$$

$$R_{eq}' = 3 + \frac{6 \times 7}{6 + 7} = 9$$


$$R_{eq}'' = 3 + \frac{6 \times 7}{6 + 7} = 3 + \frac{42}{13} = 6.2$$

$$I_1' = \frac{12}{9^3} = 1.33 \quad I_2' = \frac{7 \times 1.33}{13} = \quad I_3' = \frac{6 \times 1.33}{13}$$
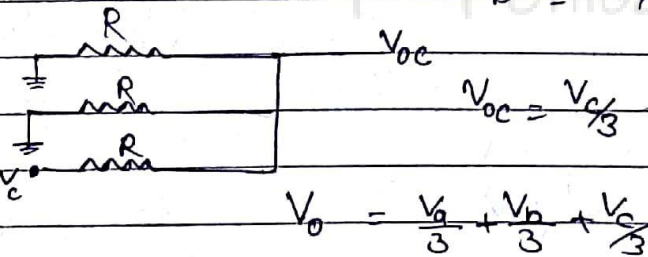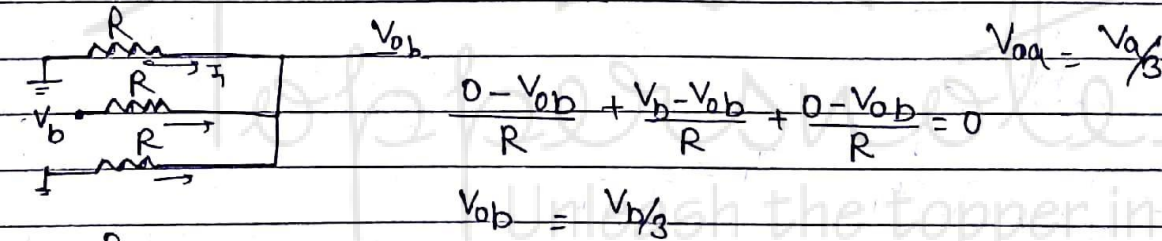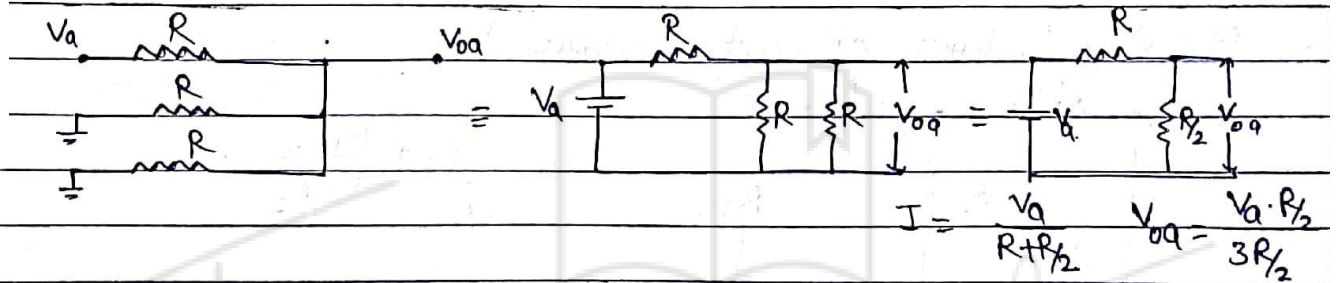
$$I_3'' = \frac{6}{6 \cdot 2} = 0.9 \quad I_1'' = \frac{6 \times 0.9}{9} = 0.6 \quad I_2'' = \frac{3 \times 0.9}{9} = 0.3$$




### Thevenin Theorem :-

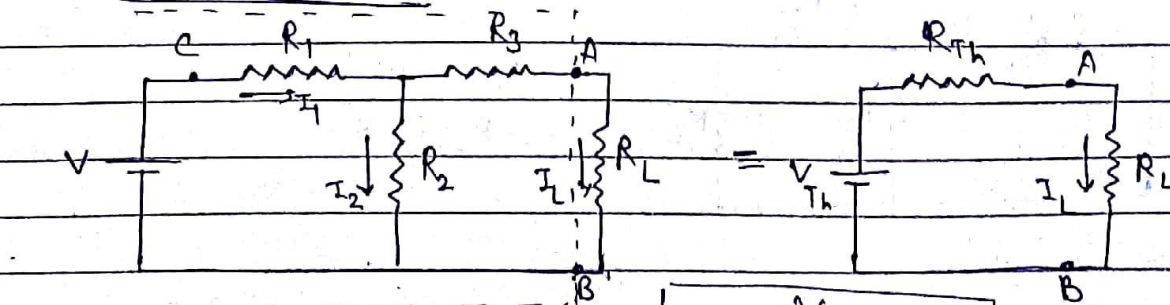

$$I_L = \frac{V_{Th}}{R_L + R_{Th}}$$
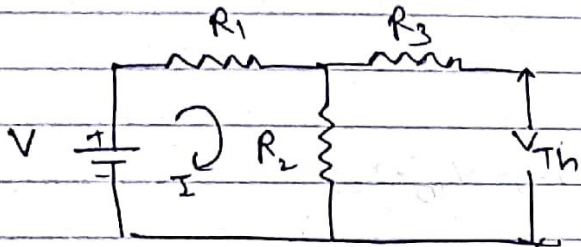
## Superposition Theorem :-


$V_{Th}$  (open circuit voltage) -  $R_1 \rightarrow \infty$



$$I = \frac{V}{R_1 + R_2}$$


$$V_{Th} = IR_3 = \frac{VR_3}{R_1 + R_2}$$

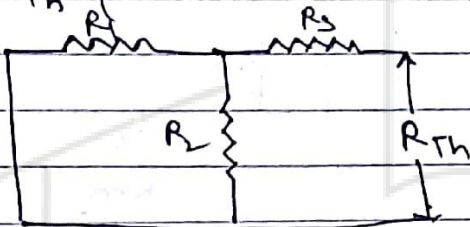Req  $R_{Th}$  (short circuit resistance)




$$R_{Th} = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$


Find  $I_1$

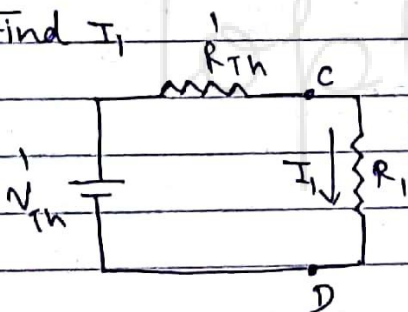

$$I_1 = \frac{V'_{Th}}{R_{Th} + R_1}$$

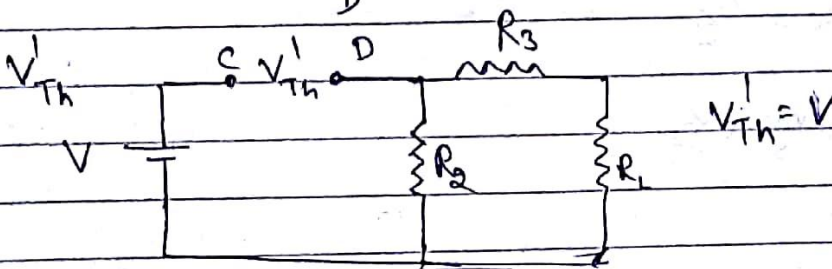


$R_{Th}$

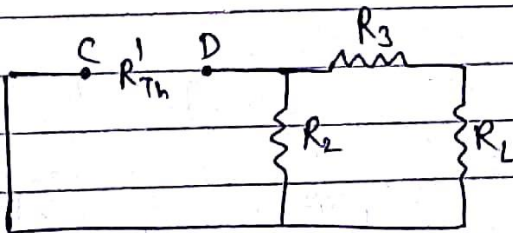


$$\frac{R_2 (R_3 + R_2)}{R_2 + R_3 + R_1}$$



Find  $I_2$  -

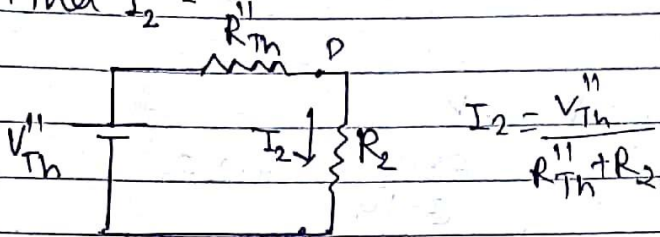

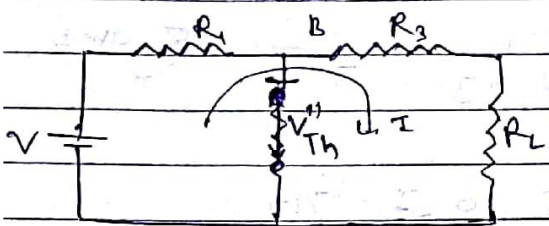
$$I_2 = \frac{V''_{Th}}{R''_{Th} + R_2}$$



$$V - (R_1 + R_3 + R_L)I = 0$$

$$I = \frac{V}{R_1 + R_3 + R_L}$$

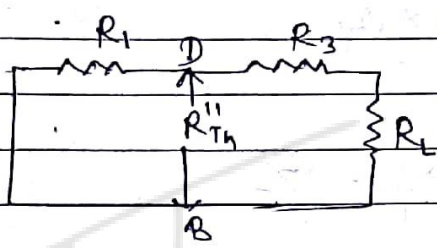


$$V''_{Th} = V - IR_1$$


$$V''_{Th} = I(R_3 + R_L)$$

$$R''_{Th} = \frac{R_1(R_3 + R_L)}{R_1 + R_3 + R_L}$$


Qn

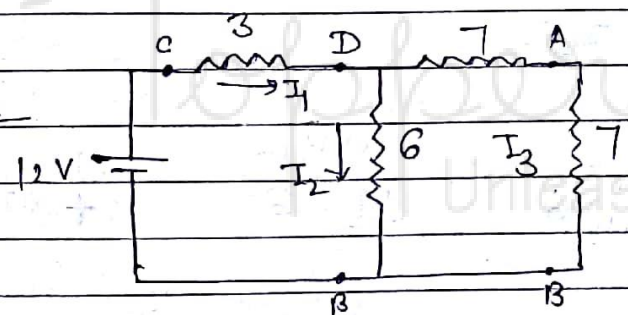


Find  $I_1, I_2, I_3$

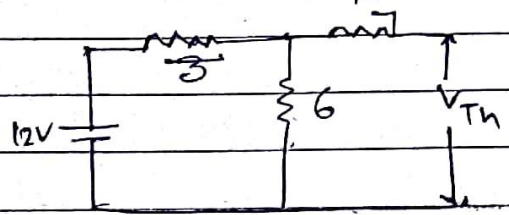


$$V_{Th} = \frac{12 \times 6}{9} = 8V$$

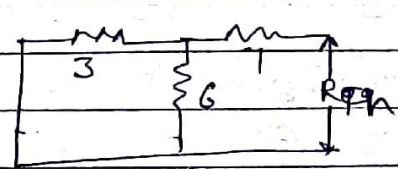
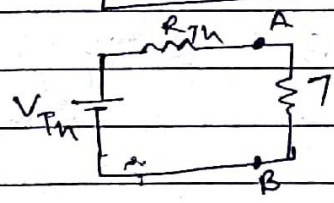
$$R_{Th} = 3 + 7 + \frac{3 \times 6}{9} = 9\Omega$$




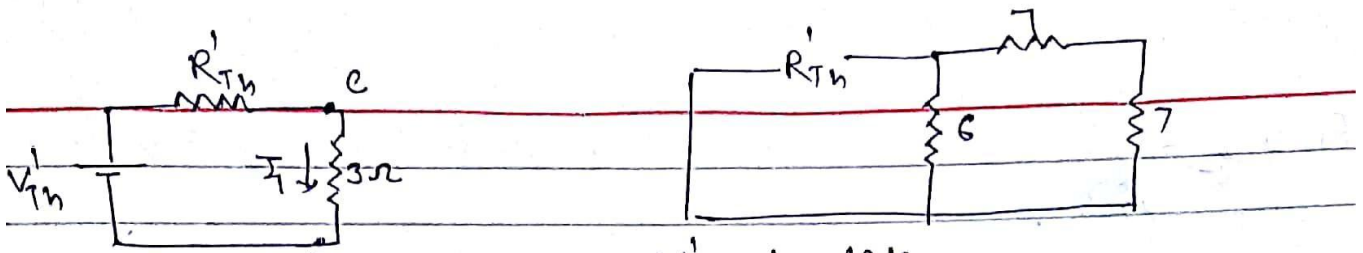
$$I_3 = \frac{V_{Th}}{R_{Th} + R_L} = \frac{8}{16} = \frac{1}{2}$$



$$V_{Th}^I = V = 12V$$


$$R_{Th}^I = \frac{6 \times 14}{6 + 14} = 4.2 \Omega$$
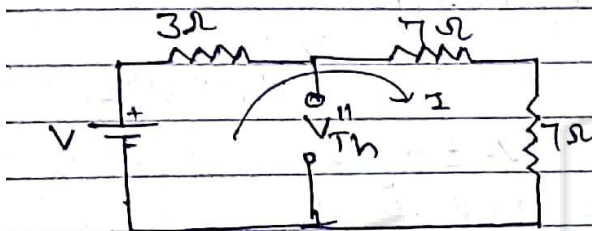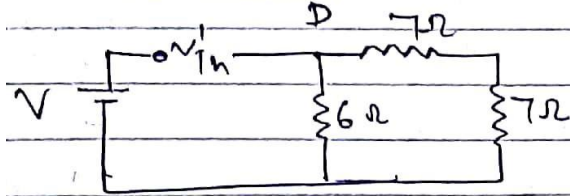
$$I_1 = \frac{V_{Th}^I}{R_{Th}^I + 3} = \frac{12}{4.2 + 3} = \frac{120}{7 \times 2.1} = \frac{5}{3} \text{ amp}$$




$$12 - 17I = 0 \quad I = 12/17$$
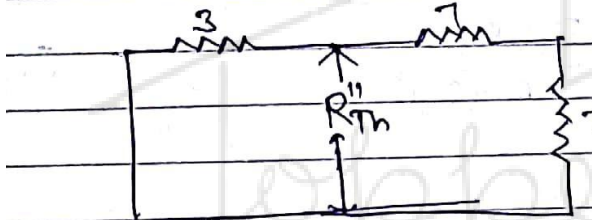
$$V_{Th}^{II} = 14 \times \frac{12}{17}$$





$$R_{Th}^{II} = \frac{3 \times 14}{17} = \frac{42}{17}$$

$$I_2 =$$

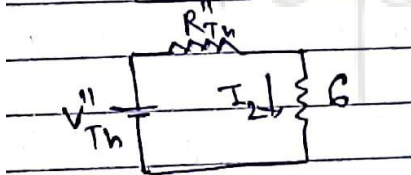

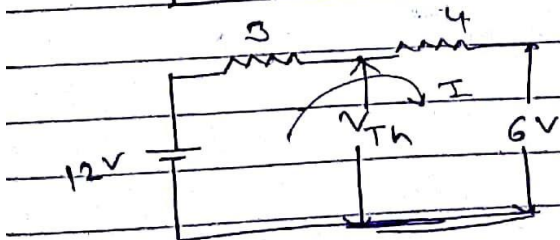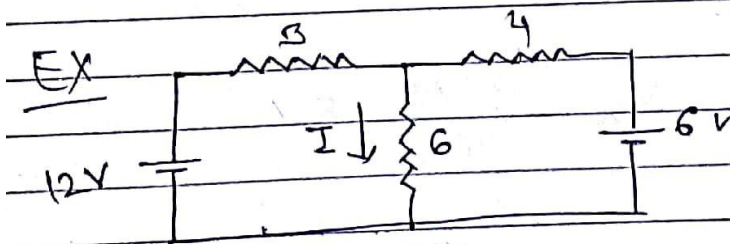
$$I_2 = \frac{V_{Th}^{II}}{R_{Th}^{II} + 6} = \frac{14 \times 12/17}{\frac{42}{17} + 6} = \frac{14 \times 12}{42 + 6 \times 17}$$




$$12 - 7I - 6 = 0$$

$$I = 6/7$$
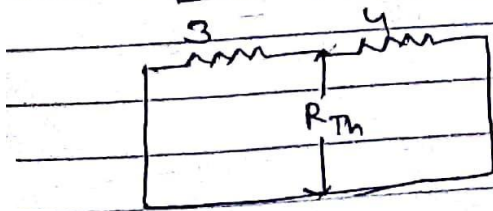
$$V_{Th} = 6 - 4 \times \frac{6}{7} = 6 - \frac{24}{7} = 6 - 3.4 = 2.6V$$





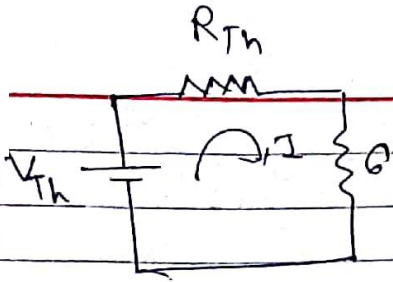
$$R_{Th} = \frac{4 \times 3}{4 + 3} = \frac{12}{7}$$




$$6 = \left(6 + \frac{12}{I}\right) I$$

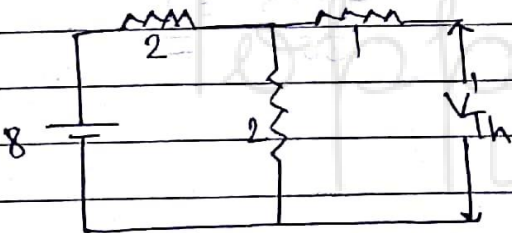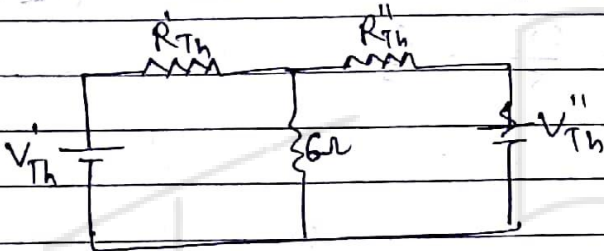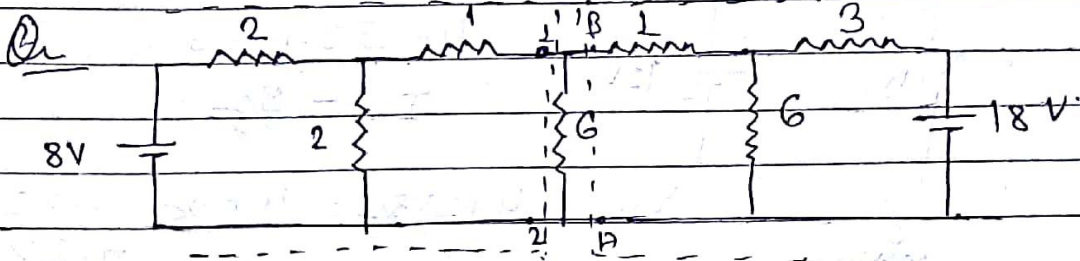
$$I = \frac{1.3}{\frac{54}{27}} = \frac{1.3 \times 27}{54} = \frac{35.1}{54} = \frac{9.1}{27} \text{ amp.}$$




$$V_{Th} = \frac{8 \times 2}{4} = 4$$

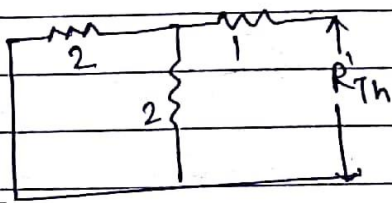



$$R_{Th}' = 3$$

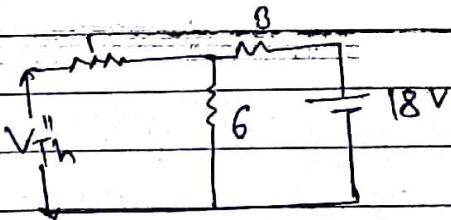

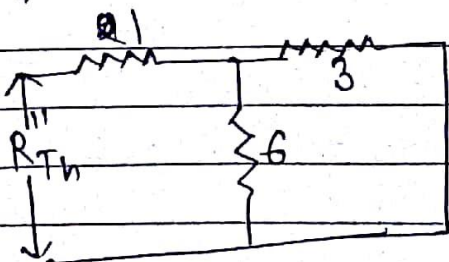
$$V_{Th}'' = \frac{18 \times 6}{9} = 12$$



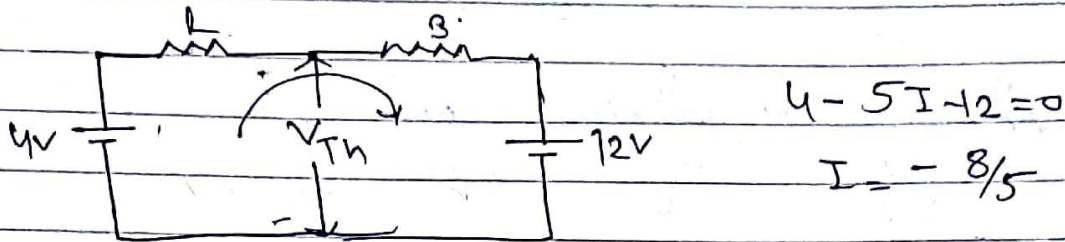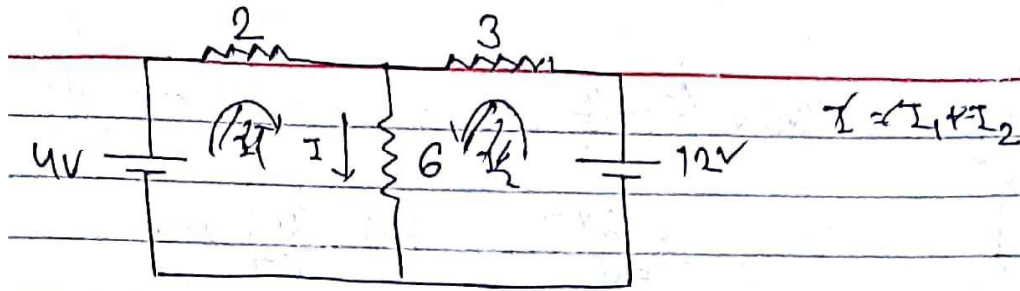
$$R_{Th}'' = 1 + \frac{3 \times 3}{9} = 3$$


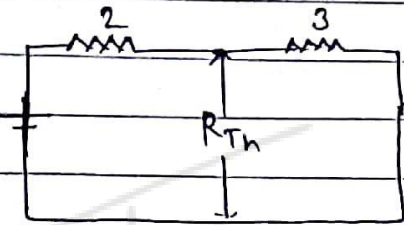
$$V_{Th} = 4 + 2 \times \frac{8}{5} = 4 + \frac{16}{5} = 4 + 3.2 = 7.2V$$



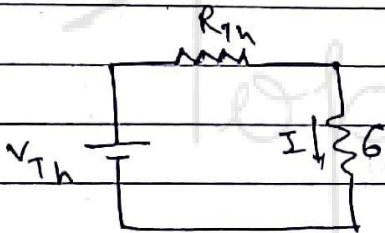
$$R_{Th} = \frac{2 \times 3}{5} = \frac{6}{5}$$




$$\frac{7.2}{\frac{6}{5} + 6} = I = \frac{7.2 \times 5}{36} = 1$$

## Norton's Theorem :-

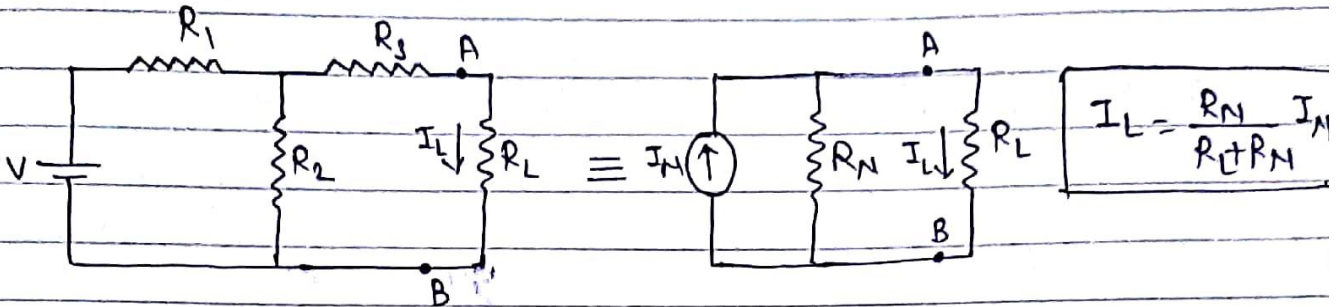


$I_N$  - short circuit current

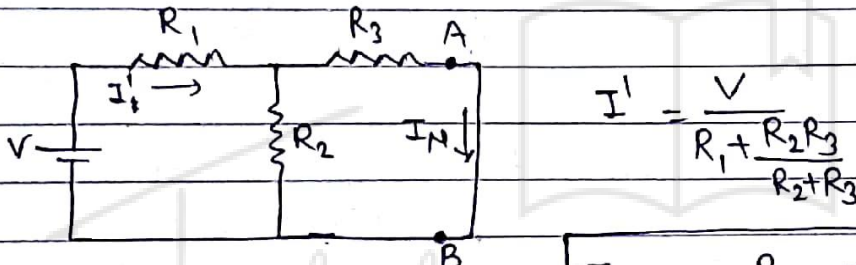


$$I' = \frac{V}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$$

$$I_N = \frac{R_2 I'}{R_2 + R_3}$$

$R_N$  (similar to  $R_{Th}$ )

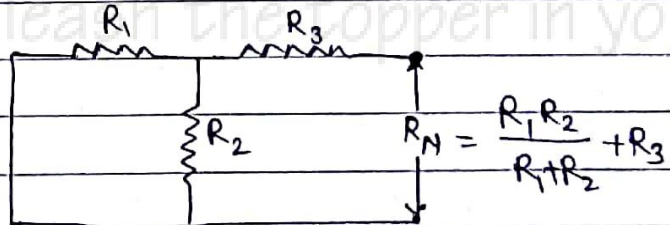
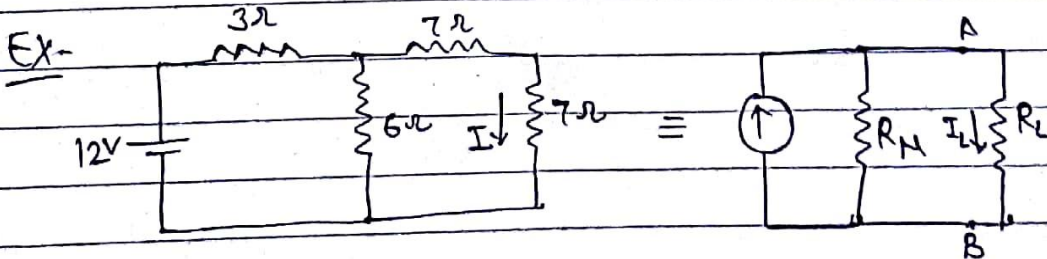
$$R_N = \frac{R_1 R_2}{R_1 + R_2} + R_3$$





$$R_N = \frac{3 \times 6}{3 + 6} + 7 = 9 \Omega$$

$$I_N = \frac{7 \times 6}{13} I'$$

$$I' = \frac{12}{3 + \frac{42}{13}} = \frac{12 \times 13}{81} = \frac{52}{9} \text{ amp.}$$

$$I_N = \frac{6}{13} \times \frac{12 \times 13}{81} = \frac{72}{81} = \frac{8}{9} \text{ amp}$$
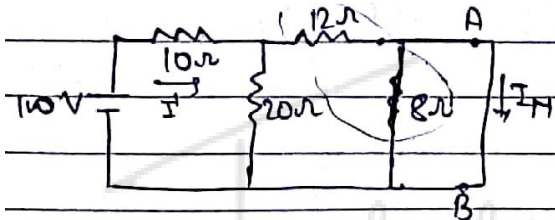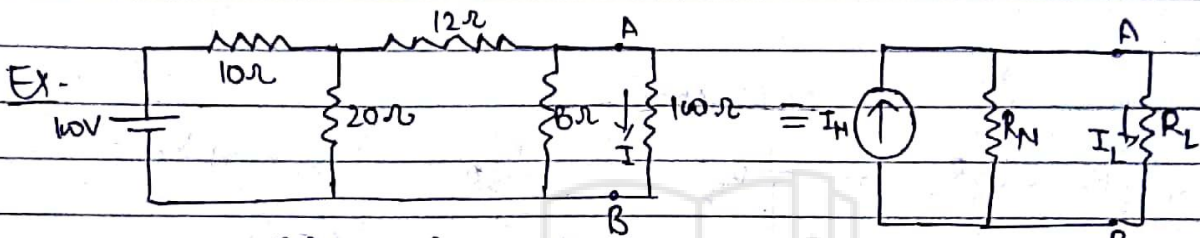
$$I_L = \frac{9}{7+9} \times \frac{72}{81} = \frac{9}{16} \times \frac{8}{9} = \frac{1}{2} \text{ amp.}$$




$$I' = \frac{100}{10 + \frac{20 \times 20}{20 + 20}} = \frac{100}{10 + \frac{240}{40}} = \frac{100}{10 + 6} = \frac{100}{16} = \frac{25}{4}$$

$$I_{N/V} = \frac{I'}{I} = \frac{100}{10+10} = 5 \text{ amp.}$$

$$I_N = \frac{20}{40} \times I' = \frac{5}{2} \text{ amp.}$$

$$R_N = 10 + \frac{20 \times 20}{40} = 10 + 10 = 20 \Omega$$

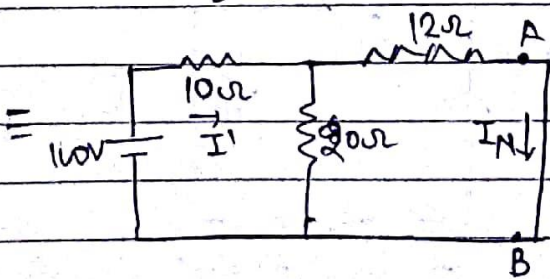
$$I_L = \frac{R_N}{R_L + R_N} I_N = \frac{20}{20 + 10} \times \frac{5}{2} = \frac{10 \times 5}{30} = \frac{5}{3} \text{ amp.}$$




$$I_1 = \frac{100}{10 + \frac{20 \times 20}{20 + 20}} = \frac{40}{7}$$

$$I_N = \frac{20}{32} I_1 = \frac{20}{32} \times \frac{40}{7} = \frac{25}{7}$$


$$R_N = 10 + \frac{20 \times 12}{32} =$$

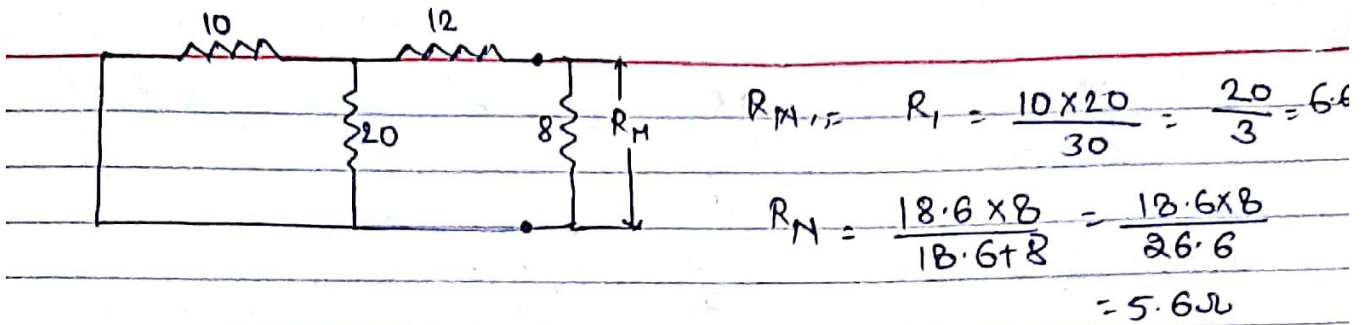


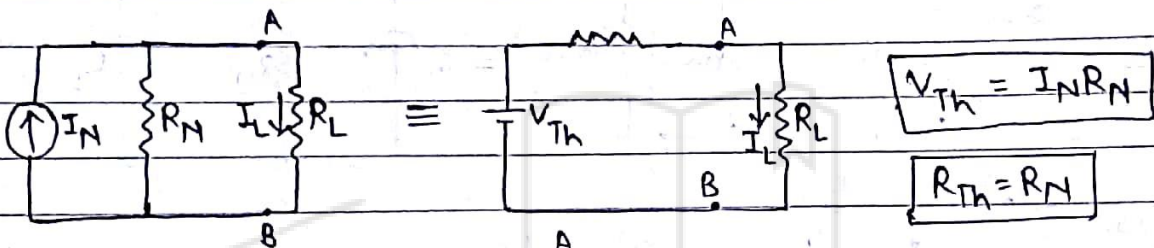
$$I_L = \frac{R_N}{R_N + R_L} I_N = \frac{5.6}{5.6 + 7} \times 25 = \frac{5.6 \times 25}{105.6} = 0.19 \text{ amp.}$$



Ex -

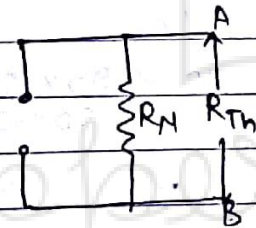


Ex -

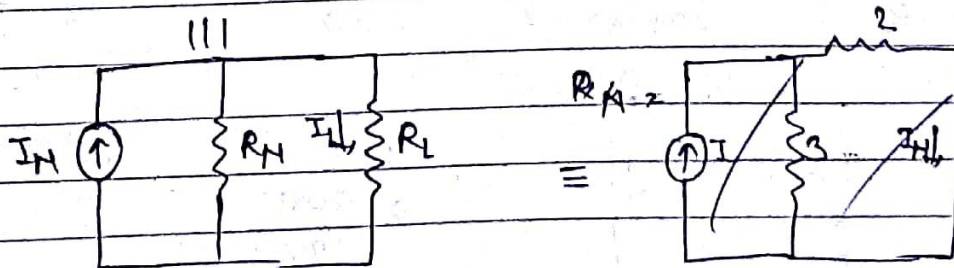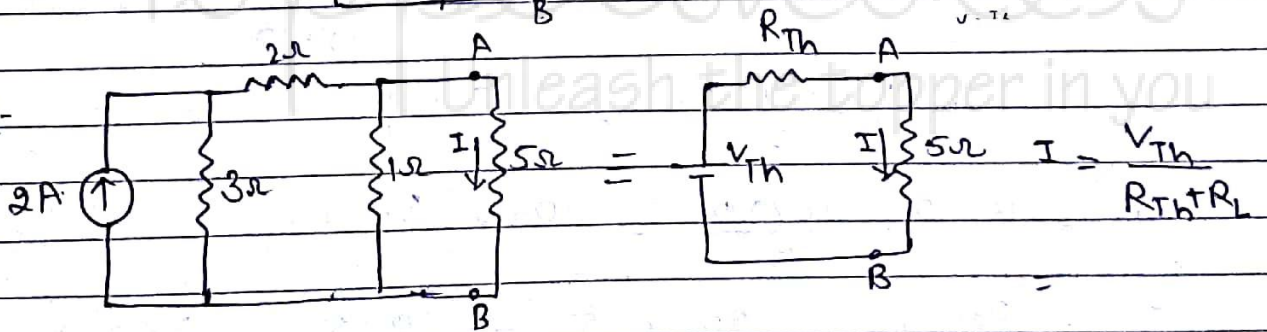


$$I_N = \frac{3}{5} \times I = \frac{3}{5} \times 2 = \frac{6}{5} \text{ amp.} \quad I_N = \frac{3}{5} \times I = \frac{3}{5} \times 2 = \frac{6}{5}$$

$R_N =$

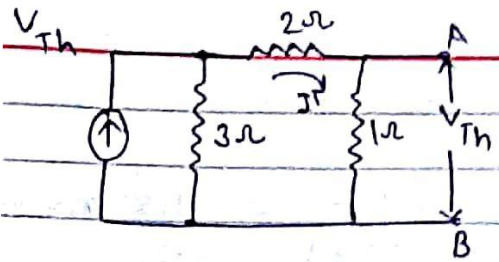

$$I' = \frac{3}{3+3} I = \frac{3 \times 2}{6} = 1 \text{ amp.}$$

$$V_{Th} = 1 \times 1 = 1 \text{ V}$$

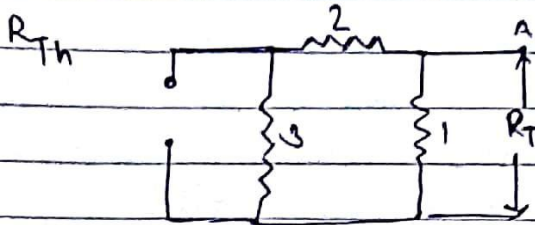



$$R_{Th} = \frac{5 \times 1}{6} = \frac{5}{6} \Omega$$

$$I = \frac{V_{Th}}{R_{Th} + R_L} = \frac{1}{\frac{5}{6} + 5} = \frac{6}{35} \text{ amp.}$$

$$V_{Th} = I_N R_N \rightarrow I_N = \frac{V_{Th}}{R_{Th}} = \frac{1}{\frac{5}{6}} = \frac{6}{5} \text{ amp.}$$

$$I_L = \frac{R_N}{R_L + R_N} I_N = \frac{\frac{5}{6}}{5 + \frac{5}{6}} \times \frac{6}{5} = \frac{6}{35} \text{ amp.}$$

$V_{Th}$  - open circuit voltage

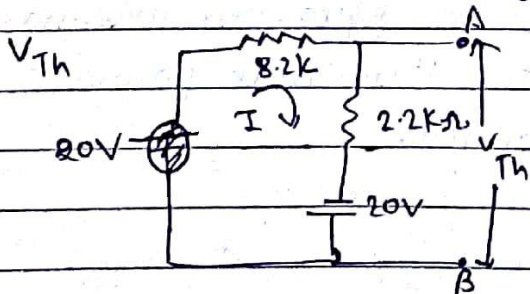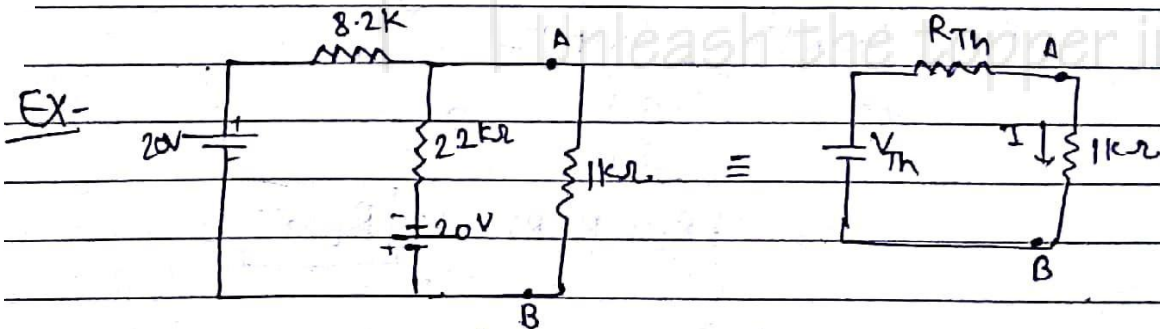

$$-20 + 8.2I + 2.2I - 20 = 0$$


$$I = \frac{40}{10.4} \text{ amp.}$$

$$V = V_{Th} - 2.2 \times \frac{40}{10.4} + 20 = 0$$

$$V_{Th} = -20 + \frac{2.2 \times 40}{10.4} + 20$$
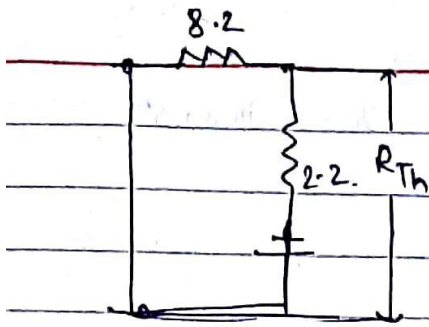
$$= -20 + \frac{20 \times 10}{52} \approx -11.5 \text{ V}$$






$$R_{Th} = \frac{8.2 \times 2.2}{8.2 + 2.2} = 1.73 \text{ k}\Omega$$

$$I = \frac{V_{Th}}{R_L + R_{Th}} = \frac{-11.5}{1.73 + 1} = \frac{-11.5}{2.73} \text{ mA}$$

### Maximum Power Transfer Theorem :-

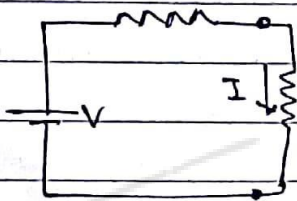

Max power transfer to the load when load resistance is equal to the internal resistance to the source

Power transfer to the load-


$$P = I^2 R_L = \frac{V^2}{(R + R_L)^2} R_L$$

$\frac{dP}{dR_L} = 0$

$$\frac{dP}{dR_L} = \frac{V^2}{(R + R_L)^2} - \frac{2V^2 R_L}{(R + R_L)^3} = 0$$

$$V^2 - \frac{1 - 2R_L}{R + R_L} = 0$$
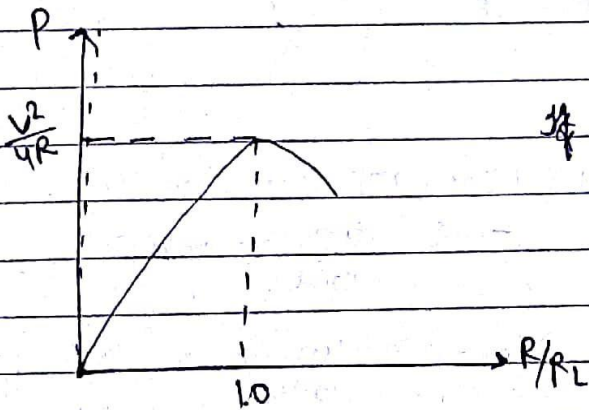
$$2R_L = R + R_L \Rightarrow \boxed{R_L = R}$$



If  $R_L$  should be equal to internal resistance then max. power will transfer.