


IES / GATE

Electrical Engineering

VOLUME-V
DIGITAL-ELECTRONICS

CONTENT

1. Combinational Logic gate	37
2. Multiplexer	44
3. Encoder	63
4. Magnitude Comparator	68
5. B.C.D Addition	75
6. Logic Families	81
7. Digital to Analog converter	102
8. Analog to Digital converter	110
9. Sequential circuits	141
10. Counters	163

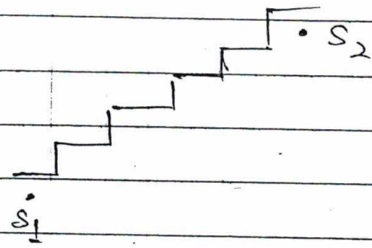

$s_2 s_1$	Bulb
0 0	0
0 1	1
1 0	1
1 1	0

$$f = s_1 \oplus s_2$$

$$\rightarrow f_7 = x + y \quad \text{OR}$$

$$x \vee y$$

$$\rightarrow f_8 = \overline{x + y} \quad \text{NOR}$$

$$\overline{x \vee y}$$

$$\rightarrow f_9 = x \ominus y \quad \text{Ex-NOR}$$

$$= x'y' + xy$$

Ex-NOR is also known as coincidence Logic or equivalence Logic Gate

$$\rightarrow f_{10} = \bar{y} \quad \text{NOT}$$

$$\rightarrow f_{11} = x + y \quad \text{Implication}$$

$$x < y \quad \text{[if } y \text{ then } x \text{]}$$






$$\rightarrow f_{12} = \bar{x} \quad \text{NOT (complementary)}$$


→ $f_{13} = \bar{x} + y$ Implication
if $x > y$ [if x then y]

→ $f_{14} = \bar{x} \cdot y$ NAND
 $x \uparrow y$

→ $f_{15} = 1$ Identity




← Symbols for the Logic Gate →

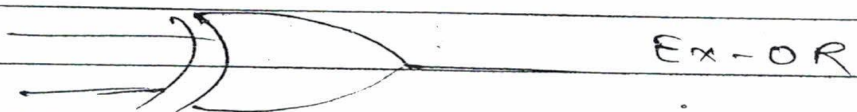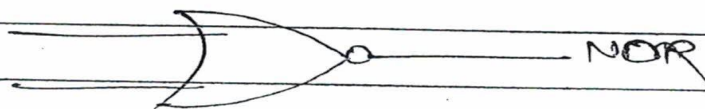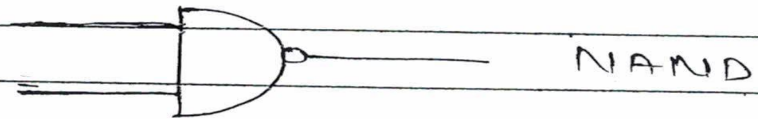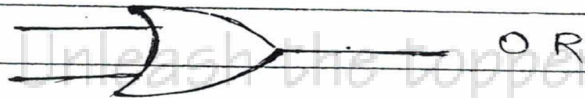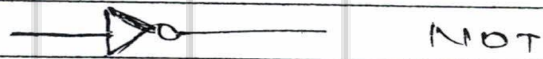

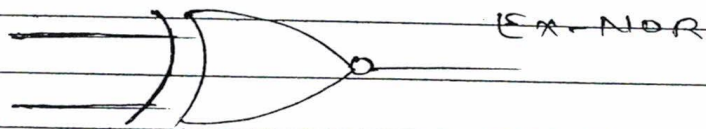

→ NOT, AND, OR are basic Logic Gates.

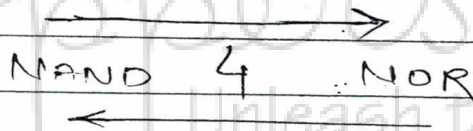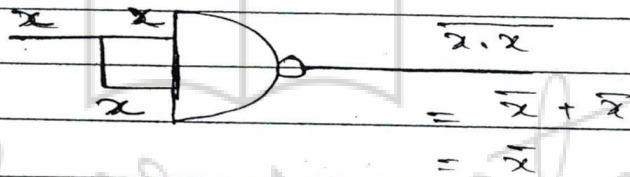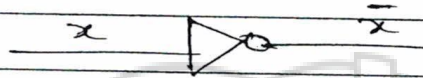→ NAND, NOR known as Universal Logic Gate.



NOT	1	1
AND	2	3
OR	3	2
EX-OR	4	5
EX-NOR	5	4

DUALITY

- Step 1) Interchange the operators, (\cdot , $+$)
- Step 2) Interchange the Identity, (0 , 1)

example
 $\rightarrow f = \bar{A} \cdot B + C$



$f^D = ?$

$f^D = (\bar{A} + B) \cdot C$

$(f^D)^D = f$

$\rightarrow x \cdot 0 = 0$

$x + 1 = 1$

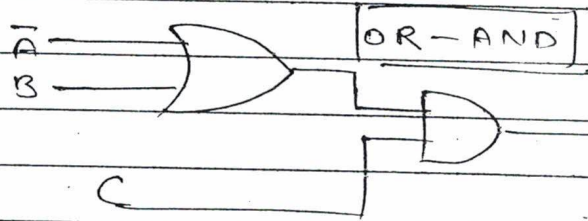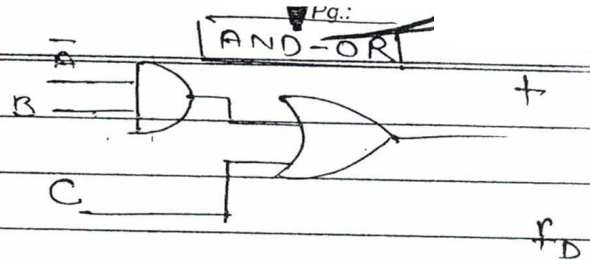

AND

OR

$x \cdot x = x$

$x \cdot 0 = 0$

$x \cdot 1 = x$

$x \cdot \bar{x} = 0$

$x + x = x$

$x + 0 = x$


$x + 1 = 1$

$x + \bar{x} = 1$


Degenerative forms

If a two level logic gate system output is expressed by a single logic gate then the two level logic Gate system is known as Degenerative forms for a single Logic Gate.

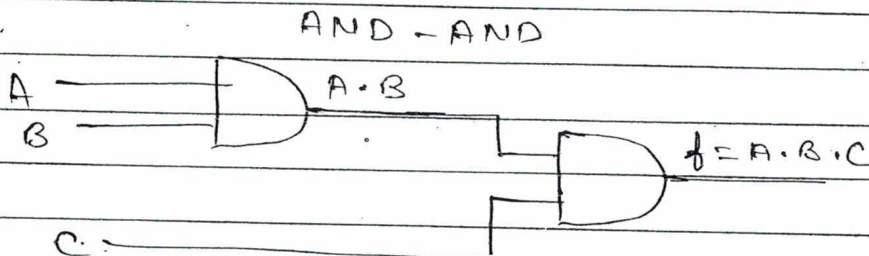Ex:- AND-AND is the degenerated form for AND Gate.




AND

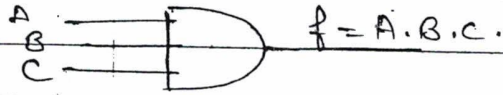


Non-Degenerative forms

OR-AND

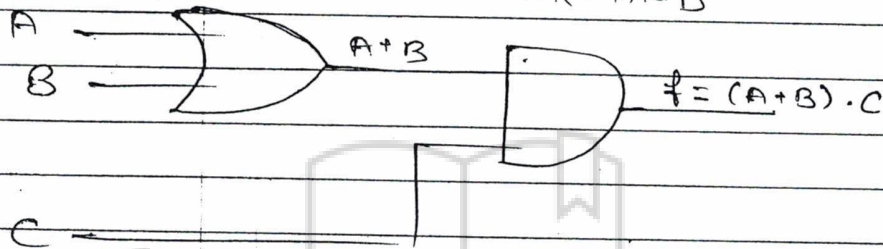

List of Non-Degenerative forms.

Equivalent	AND-OR NAND-NAND NOR-OR OR-NAND	OR-AND NOR-NOR NAND-AND AND-NOR	Equivalent
------------	--	--	------------



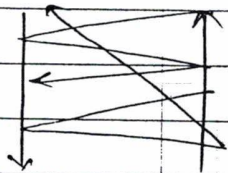


In the above Representation of Non-Degenerative List combination of the same horizontal line are 'dual forms.

eg.

AND-OR dual is OR-AND

→ Alternative Logic Gate

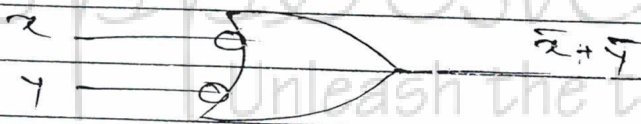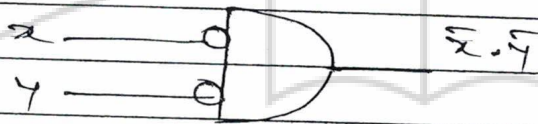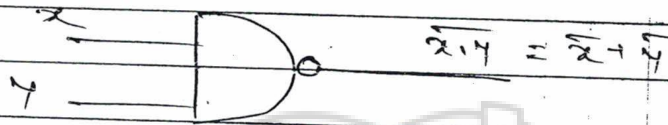

Bubbled

NAND	→	OR
NOR	→	AND
AND	→	NOR
OR	→	NAND

$$\begin{aligned} \overline{x \cdot y} &= \overline{x} + \overline{y} \\ \overline{x + y} &= \overline{x} \cdot \overline{y} \end{aligned}$$

→ Positive Negative Logics

(+)ve Logic
 High → 1
 Low → 0

(-)ve Logic
 High → 0
 Low → 1

(+)ve Logic
 -2V → 1
 -7V → 0


(+)ve AND logic


A	B	f = A · B
0	0	0
0	1	0
1	0	0
1	1	1

(-)ve AND logic = (+)ve OR Logic

A	B	f
1	1	1
1	0	1
0	1	1
0	0	0

→ Inhibit Input of Logic Gate

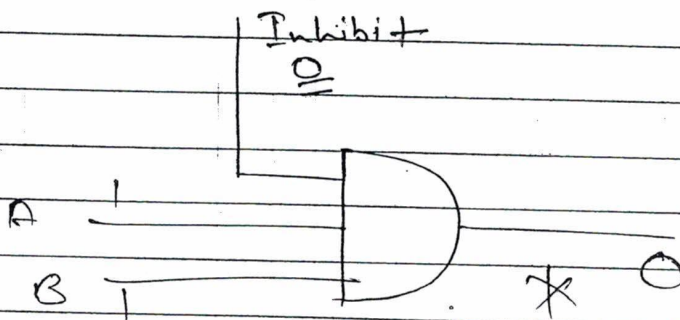

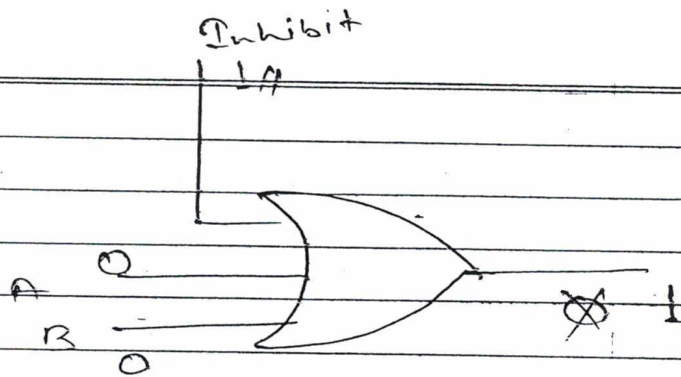

Inhibit

Disable : Enable

	Disable	Enable
NAND	L	H
NOR	H	L
AND	L	H
OR	H	L

Imp. X-OR (Imp.)

$x \oplus x$	$x = 0$	
$x \oplus \bar{x}$	$\bar{x} = 1$	$x \oplus 1 = \bar{x}$
$x \oplus 1$	$1 = \bar{x}$	$\bar{x} \cdot 1 + x \cdot \bar{1}$
$x \oplus 0$	$0 = x$	$= \bar{x} \cdot 1 + 0 = \bar{x}$

$x \odot x$	$x = 1$
$x \odot \bar{x}$	$\bar{x} = 0$
$x \odot 1$	$1 = x$
$x \odot 0$	$0 = \bar{x}$

$$\left. \begin{array}{l} x \oplus y \\ x \oplus y' \\ x' \oplus y \end{array} \right\} x \odot y$$

$$\begin{aligned}
 x \oplus y &= x'y' + x(y')' \\
 &= x'y' + xy \\
 &= x \odot y
 \end{aligned}$$

$$x \oplus y = x \ominus y$$

$$x \oplus y \oplus z = x \ominus y \ominus z$$

$$w \oplus x \oplus y \oplus z = w \ominus x \ominus y \ominus z$$

For even variable (Bar = NOT)

For odd variable (Ex-OR = Ex-NOR)

→ Complementing the boolean expression

Step 1) Duality

Step 2) Compling the individual variable

Eg!

$$f = A'B + C$$

$$f' = ?$$

1. $(A' + B) \cdot C$

2. $(A + B') \cdot C' = f'$

→ Order of Operators



1. []

2. NOT


3. AND

4. OR


← Venn Diagrams →

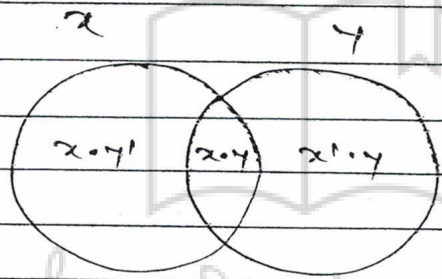
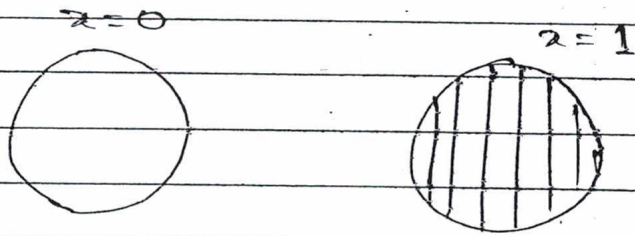


→ $x + x \cap y = x$

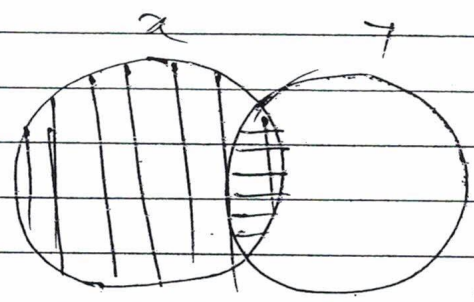

⇒ $x + x \cap y = x + y$

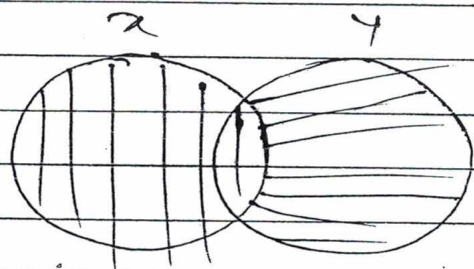

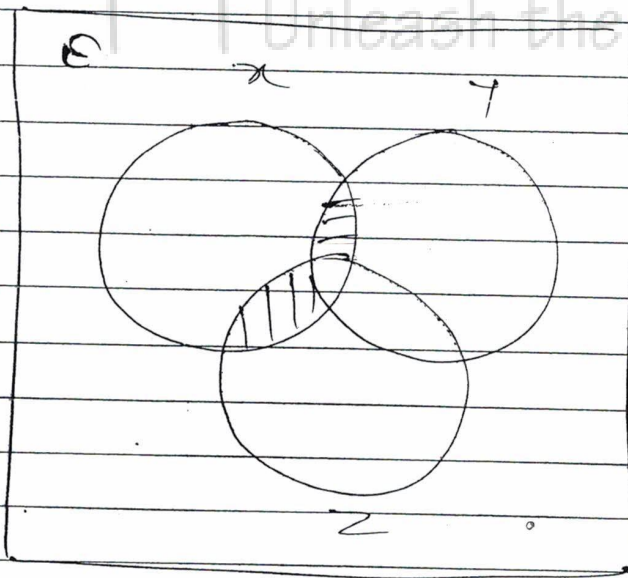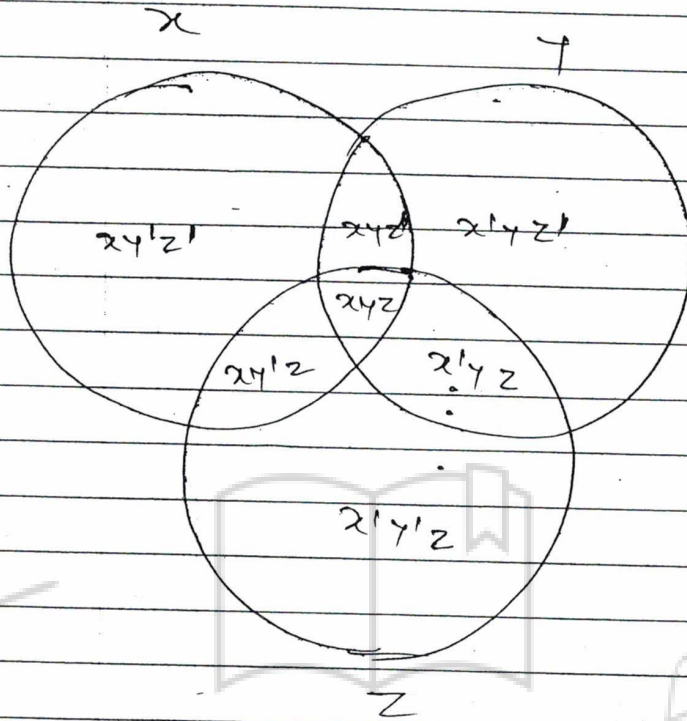

$$f = E \cdot (xy'z' + xy'z)$$

→ Logic minimization Techniques.

NOT

if $x = 0$

$\bar{x} = 1$

$(x')' = x$

Boolean Law

AND

$x \cdot x = x$

$x \cdot \bar{x} = 0$

$x \cdot 1 = x$

$x \cdot 0 = 0$

OR

$x + x = x$

$x + 1 = 1$

$x + 0 = x$

$x + \bar{x} = 1$

Commutative Law

$x \cdot y = y \cdot x$

$x + y = y + x$

Associative Law

$(x \cdot y) \cdot z = x \cdot (y \cdot z)$

$(x + y) + z = x + (y + z)$

$$1 + B + C = 1$$

$$1 + \bar{C} + CD + \bar{C}\bar{D}E = 1$$

Distributive Law

$$x \cdot (y + z) = x \cdot y + x \cdot z$$

$$x + (y \cdot z) = (x + y) \cdot (x + z)$$

De Morgan's Law

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

$$\overline{\bar{x} + \bar{y}} = x \cdot y$$

Consensus Theorem

A variable is associated with some variable & its complement is associated with another variable then the next term is formed by the left over variable then the term becomes Redundant.

$$A \cdot B + \bar{A} \cdot C + \textcircled{B \cdot C} = A \cdot B + \bar{A} \cdot C$$

\Downarrow
 Redundant



$$A \cdot B + \bar{A} \cdot C + \textcircled{BCDE} = A \cdot B + \bar{A} \cdot C$$

$$(A + B) \cdot (\bar{A} + C) \cdot (B + C) = (A + B) \cdot (\bar{A} + C)$$

Transposition Theorem

$$A \cdot B + \bar{A} \cdot C = (A + C) \cdot (\bar{A} + B)$$

$$(A + B) \cdot (\bar{A} + C) = (A \cdot C) + (\bar{A} \cdot B)$$

operators & association can be interchange.

Absorption Law

OR in the variable with ANDing of that variable with another variable result in the same variable.

$$x + x \cdot y = x$$

$$x \cdot (x + y) = x$$

Redundant Lateral Rule

ORing of a variable with ANDing of its component by another variable results in the ORing of those two variable.

16

$$x + x \cdot y = x + y$$

$$x \cdot (x + y) = x \cdot y$$


SOP & POS forms

SOP (Σm)

	x	y	minterm	f
0	0	0	$\bar{x} \cdot \bar{y}$	0
1	0	1	$\bar{x} \cdot y$	1
2	1	0	$x \cdot \bar{y}$	0
3	1	1	$x \cdot y$	1

$$f = \Sigma m(1, 3) = \Pi M(0, 2)$$
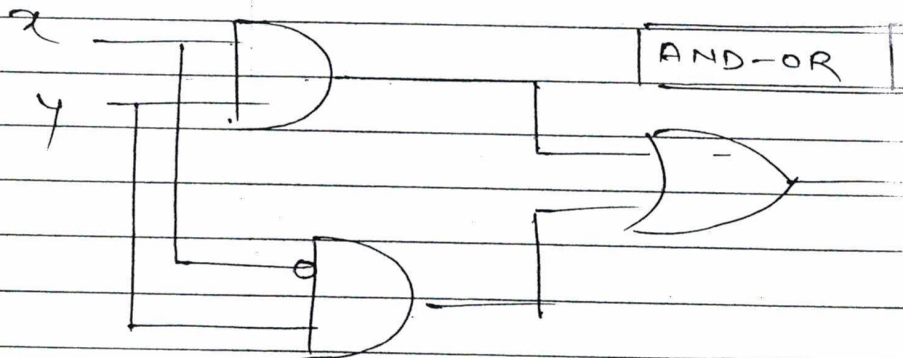
$$f = x \cdot y + \bar{x} \cdot \bar{y}$$



→ Half Adder

0	0	1	1	1
0	1	0	1	1
0	1	1	0	0

x	y	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$\begin{aligned} \text{sum} &= \bar{x} \cdot y + x \cdot \bar{y} \\ &= x \oplus y \end{aligned}$$

$$\text{Carry} = x \cdot y$$

