

IES / GATE

Electrical Engineering

VOLUME-IX


Power System-II

CONTENT

1. Power Analysis of AC – circuit	1
2. Unsymmetrical Fault Analysis	90
3. Fault Analysis using Z_{BUS}	136
4. Load Flow Analysis	156
5. Transient Stability	201

* Power analysis of A.C. circuit -

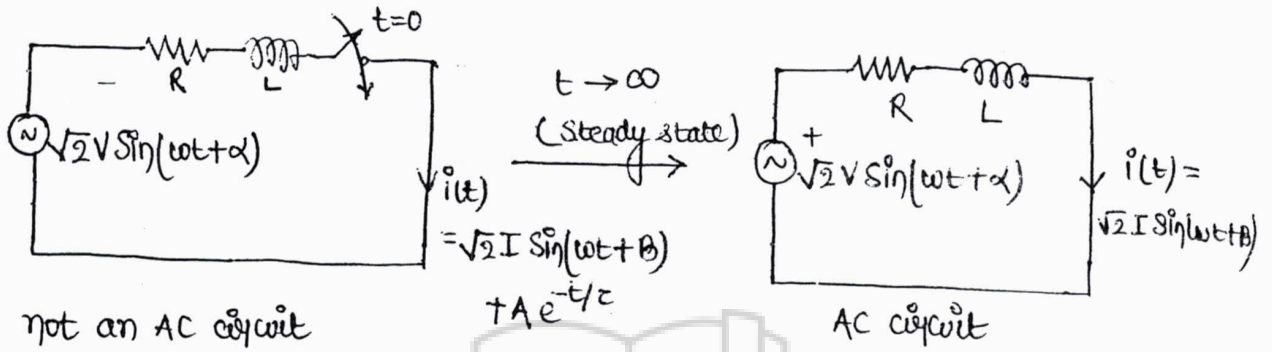A circuit which is in steady state corresponding to a given sinusoidal excitation is called AC circuit.




Responses are non-sinusoidal

Responses are sinusoidal.

> All the responses of an AC circuit are sinusoids with frequency equal to the source frequency.
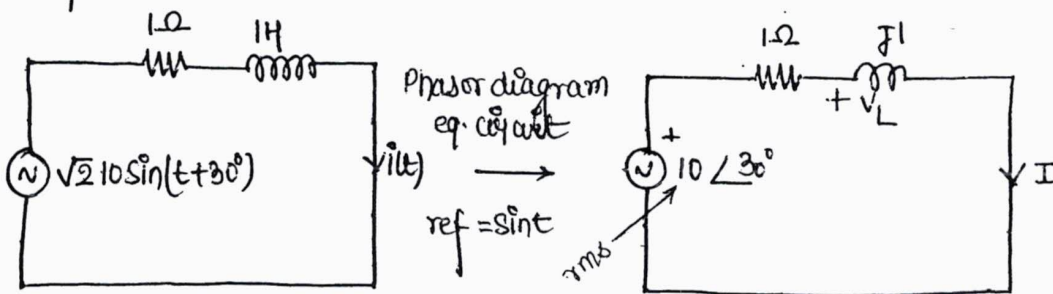
> The magnitude & phase of the response in an AC circuit is determined by phasor technique.




$$i(t) = 10 \sin(t - 15^\circ)$$

$$I = \frac{10 \angle 30^\circ}{1 + j1} = \frac{10}{\sqrt{2}} \angle -15^\circ$$

$$V_L = \left(\frac{j1}{1 + j1} \right) 10 \angle 30^\circ$$
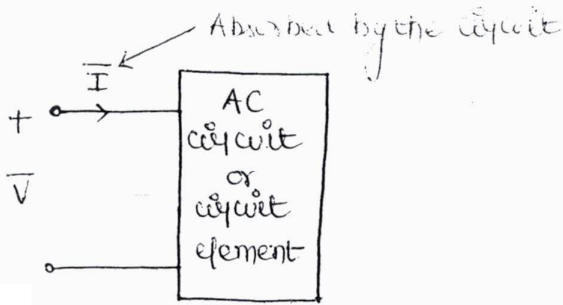
$$= \frac{10}{\sqrt{2}} \angle 75^\circ$$



Complex power absorbed by the circuit or circuit element

$$S = VI^* = P + jQ$$

$P \rightarrow$ Active power / useful power / Avg. power / power absorbed by the ckt or ckt. element (watt)
 $Q \rightarrow$ Reactive power / lagging VAR absorbed by the circuit or ckt. element (VAR).

$P > 0 \rightarrow$ ckt. absorbs active power


$P < 0 \rightarrow$ ckt. delivers active power

$Q > 0 \rightarrow$ ckt. absorbs reactive power or lagging VAR or lagging current.
 or

circuit delivers leading VAR / leading current

$Q < 0 \rightarrow$ circuit delivers reactive power / which is lagging VAR / lagging current
 or

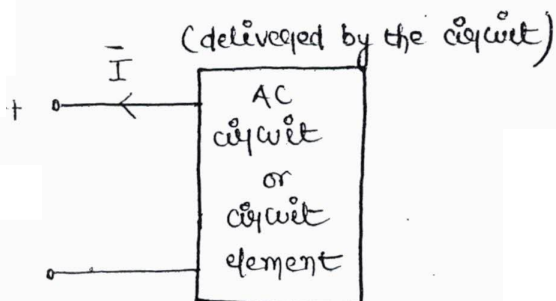The circuit absorbs leading VAR / leading current



Complex power delivered by the circuit or circuit element -

$$S = VI^* = P + jQ$$

$P \rightarrow$ Active power delivered by the circuit or circuit element


$Q \rightarrow$ Reactive power delivered by the circuit or circuit elements

$P > 0 \rightarrow$ circuit delivers active power

$P < 0 \rightarrow$ circuit absorbs active power

$Q > 0 \rightarrow$ circuit delivers reactive power

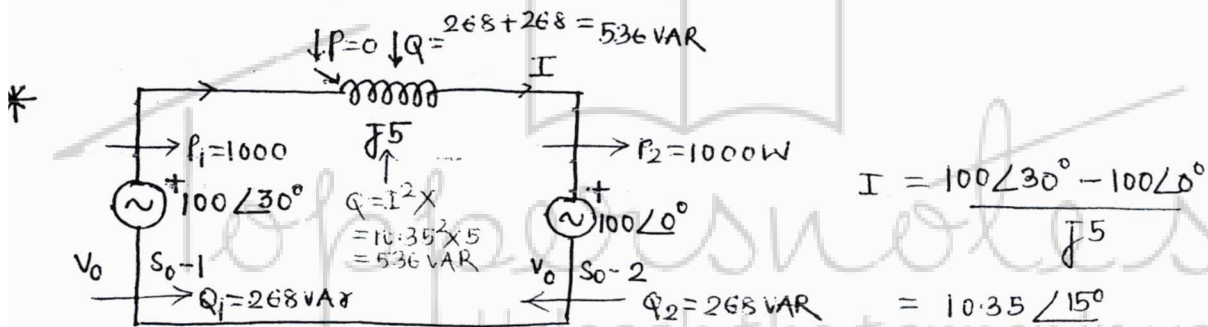$Q < 0 \rightarrow$ circuit absorbs reactive power



Complex power absorbed by V.S.2

$$S_2 = (100\angle 0^\circ)(10.35\angle 15^\circ)^* = 1000 - j268$$

V.S.2 \rightarrow


Absorbs 1000W & delivers 268 VAR

V.S.1 \rightarrow


Complex power absorbed by V.S.1

$$S_1 = (100\angle 30^\circ)(10.35\angle 15^\circ)^* = 1000 + j268$$

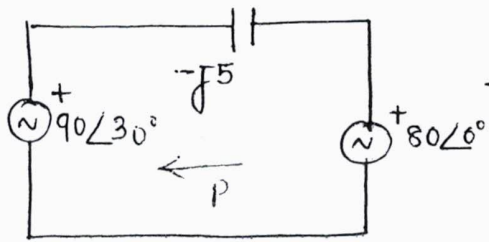Voltage source-1. delivers 1000W & 268 VAR.




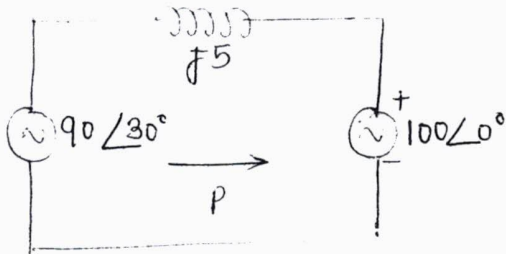→ not a practical power system circuit.
capacitor not connected in series



Reactive power generally* flows from higher to low value.
* But not always.

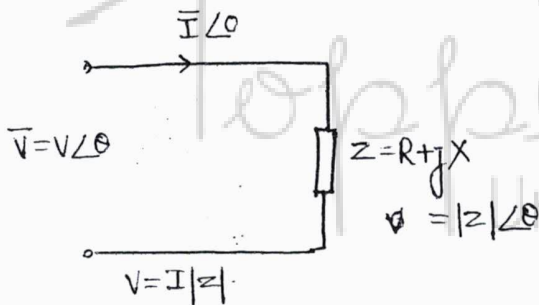In power system (with inductive series branch) active power always flows from leading voltage source towards lagging voltage source.



$$|Z| = \sqrt{R^2 + X^2}$$


$$\theta = \tan^{-1} \frac{X}{R}$$

Complex power absorbed by $Z = R + jX$

$$S = \bar{V} \bar{I}^* = V I \angle \theta = P + jQ$$

$$P = V I \cos \theta = V I \frac{R}{|Z|} = I^2 R$$


$$Q = V I \sin \theta = V I \frac{X}{|Z|} = I^2 X$$

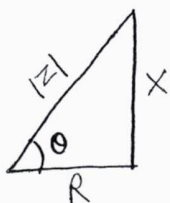

$$\cos \theta = \frac{R}{|Z|}$$

$$\sin \theta = \frac{X}{|Z|}$$

Impedance Triangle

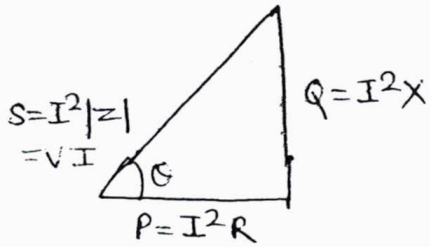




$$\text{P.f.} = \cos \theta = \frac{P}{S}$$

$R \gg 0 \Rightarrow P \gg 0$ ($z = R + jX$ can't deliver active power)

$X > 0$ (Inductive) $= Q > 0$ Inductive circuit absorbs reactive power

$X = 0$ (Resistive) $= Q = 0$

$X < 0$ (Capacitive) $\Rightarrow Q < 0$ capacitive ckt. delivers reactive power.

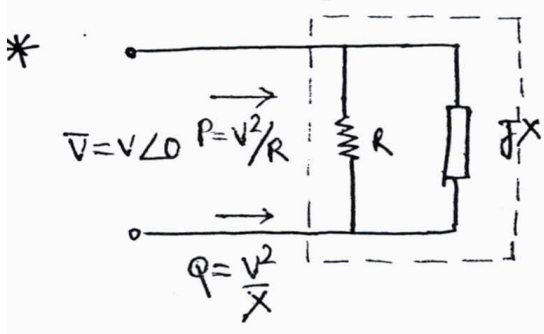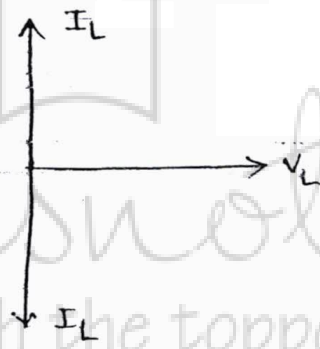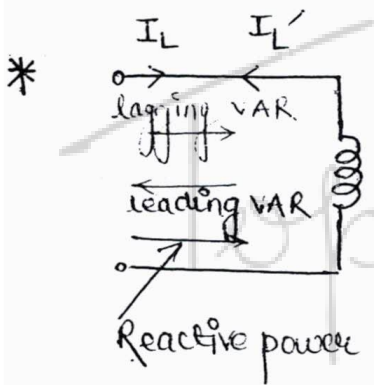


Balance 3- ϕ circuit / concept of phase sequence

A polyphase system is said to be balance if

- > The magnitude of corresponding quantities are equal in each phase.
- > The phase difference between corresponding quantities is given by θ .

$$\theta = \frac{360^\circ}{n} \rightarrow n \neq 2$$


$$90^\circ \rightarrow n = 2$$


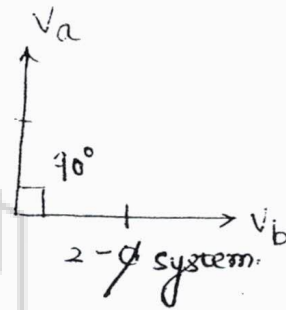


The currents in two phases of a 2- ϕ system is given below. Find the relation between ϕ_1 & ϕ_2 so that these current represents a balance 2- ϕ system.



$$i_a = \sqrt{2} I \sin(\omega t - \phi_1)$$
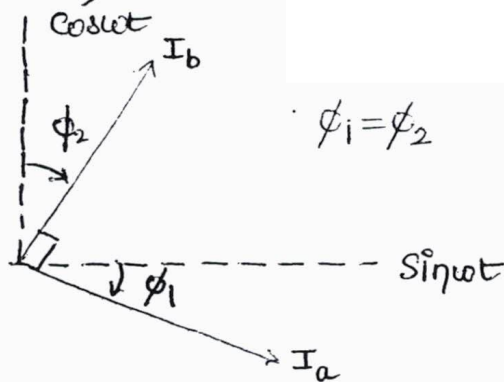
$$i_b = \sqrt{2} I \cos(\omega t - \phi_2)$$





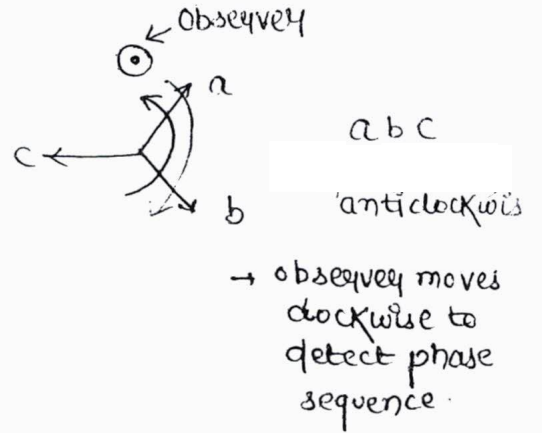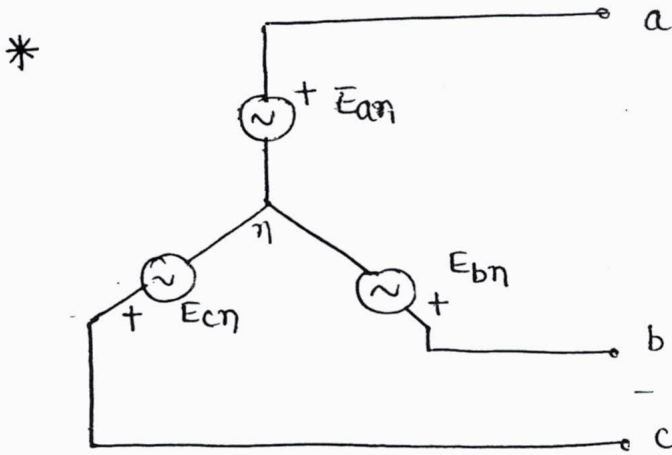


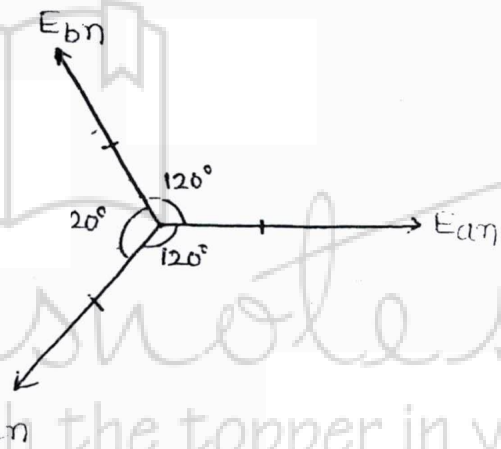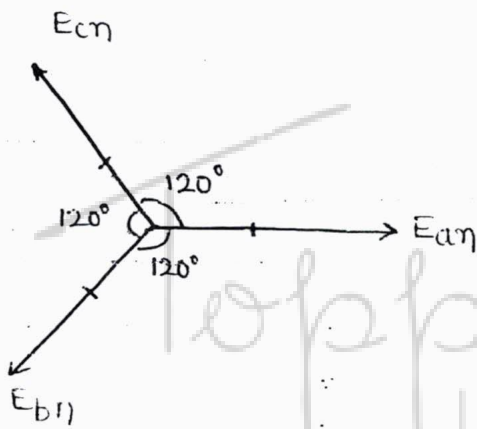→ The 3- ϕ voltage source represents a synchronous machine.




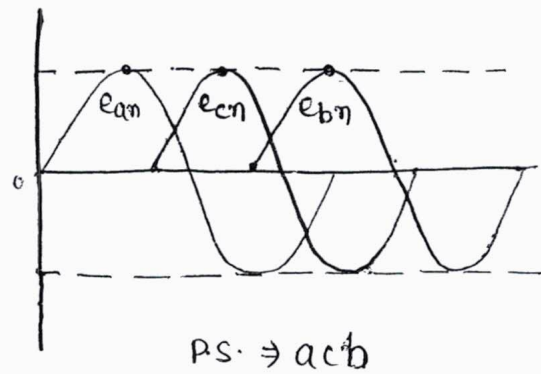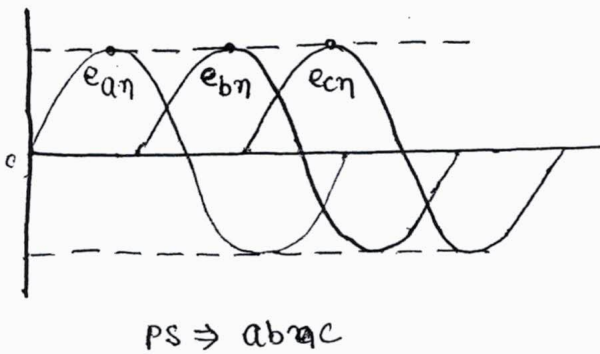→ Both phasor diagram represents balance condition but they do differ in phase sequence.



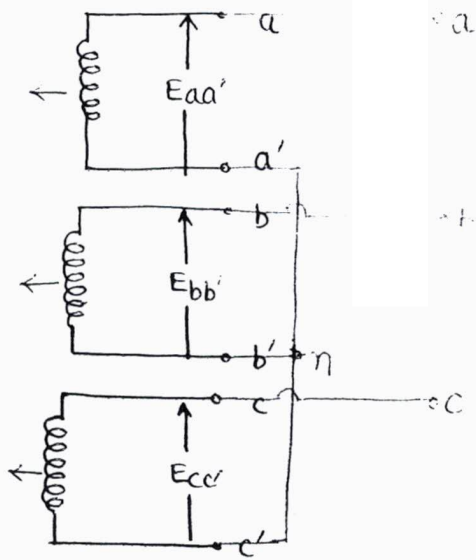

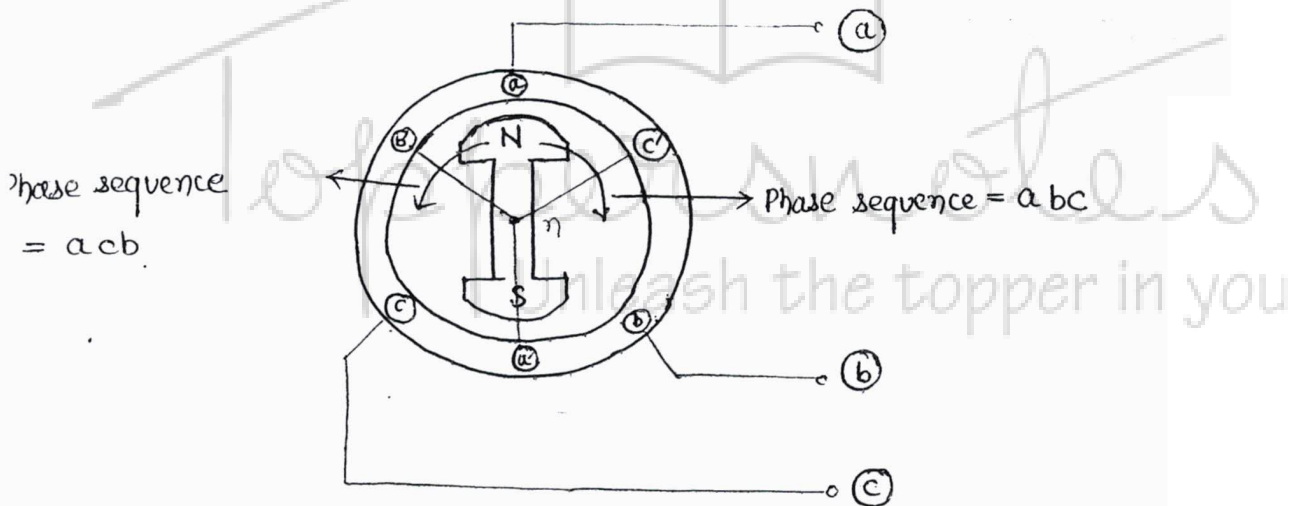Identical winding for all three phases to produce equal magnitude of voltage in all three phases.




$$\Theta_e = \frac{P}{2} \Theta_M$$

Only two type of phase sequence (abc & acb) is possible in 3- ϕ system. Theoretically phase sequence can be reversed by reversing the direction of rotation of the rotor but practically this is not feasible.


→ If field winding excitation is reversed phase sequence will not reversed.

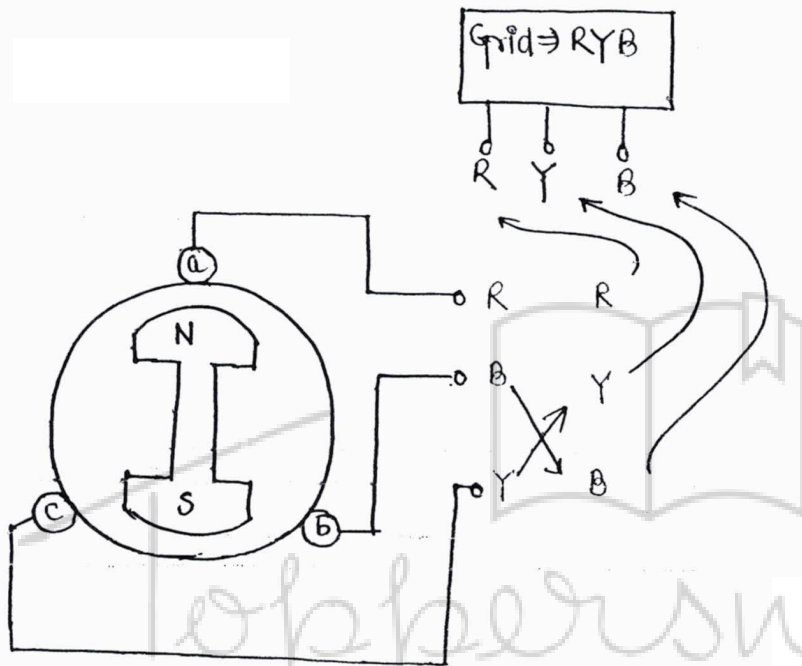* Phase sequence of the machine is practically reversed by interchanging any two terminals of a machine.



In a particular power system all the machines operates at same phase sequence & it is the sequence of whole system.

* Analysis of Balance 3- ϕ circuit

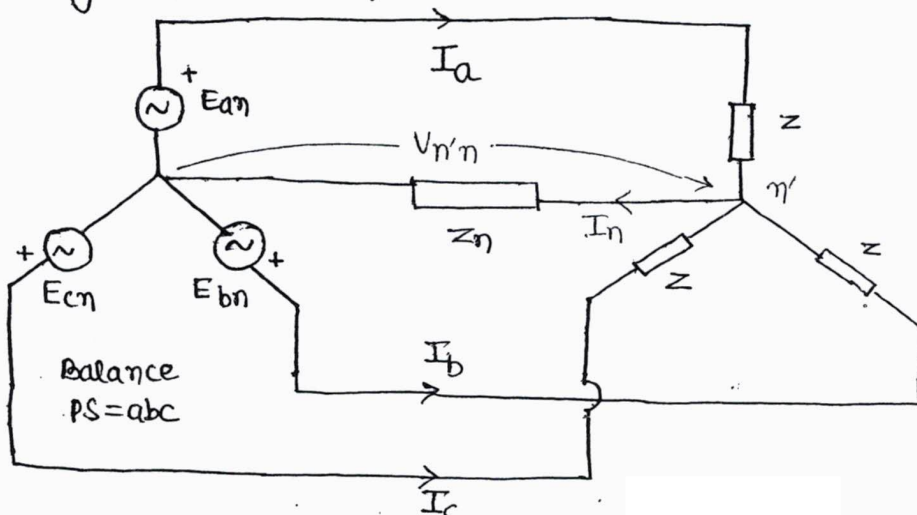

$$I_a + I_b + I_c - I_n = 0$$

$$\frac{E_{an} - V_{n'n}}{Z} + \frac{E_{bn} - V_{n'n}}{Z} + \frac{E_{cn} - V_{n'n}}{Z} - \frac{V_{n'n}}{Z_n} = 0$$

$$\frac{1}{Z} (E_{an} + E_{bn} + E_{cn}) - \left(\frac{3}{Z} + \frac{1}{Z_n} \right) V_{n'n} = 0$$

Since, the source is balanced

$$E_{an} + E_{bn} + E_{cn} = 0 \Rightarrow V_{n'n} = 0$$

$$I_n = 0$$

$$I_a = \frac{E_{an}}{Z}$$

$$I_b = \frac{E_{bn}}{Z}$$

$$I_c = \frac{E_{cn}}{Z}$$

$$E_{an} = 100 \angle 0^\circ$$

$$E_{bn} = 100 \angle -120^\circ$$

$$E_{cn} = 100 \angle 120^\circ$$

P.S. = abc
 $Z = 10 \angle 30^\circ$

$$I_a = \frac{E_{an}}{Z} = \frac{100 \angle 0^\circ}{10 \angle 30^\circ} = 10 \angle -30^\circ$$

$$I_b = \frac{E_{bn}}{Z} = \frac{100 \angle -120^\circ}{10 \angle 30^\circ} = 10 \angle -150^\circ$$


$$I_c = \frac{E_{cn}}{Z} = \frac{100 \angle 120^\circ}{10 \angle 30^\circ} = 10 \angle 90^\circ$$

PS = abc

*In a balance 3- ϕ circuit

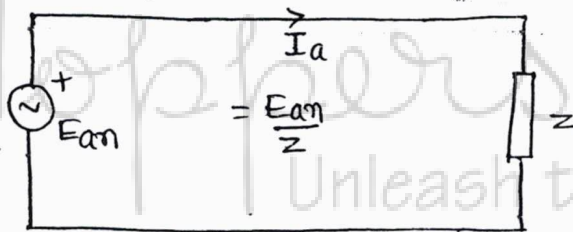- i) All the responses are balance if they have phase sequence as of the sources in the circuit.
- ii) All the neutrals are at same potential & hence there will be no current in the neutral connection irrespective of the value of Z_n .
Hence the neutral connection can be replaced by O.C. or S.C. but we prefer S.C. to show the fact that neutrals are at same potential.
- iii) All the three phases are decoupled i.e. independent of each other hence the analysis can be done on individual phase basis.



→ For the analysis of phase 'a' of the balance circuit phase A equivalent circuit drawn as follows:-



Phase-a equivalent circuit / per phase eq circuit

If phase-a quantity is computed from phase-a equivalent circuit phase-b & phase-c quantities can be determined directly with the help of phase sequence of the source.

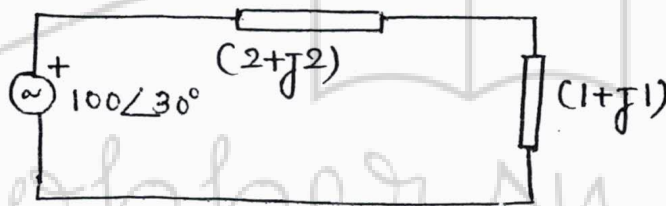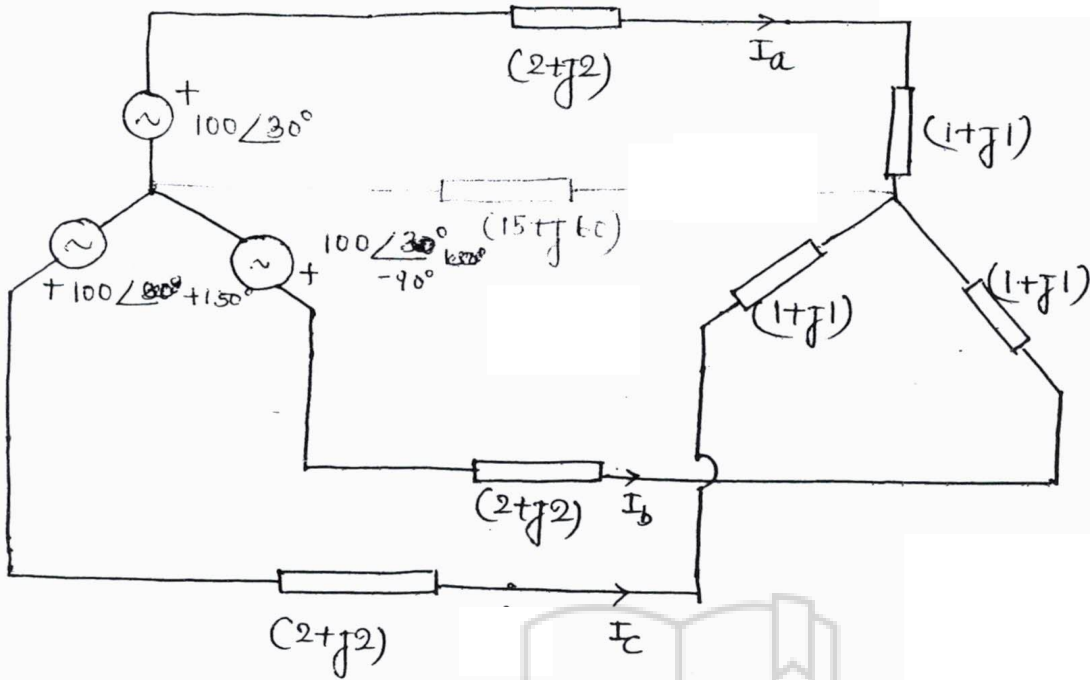"The analysis of a balance 3- ϕ circuit is always done on per phase basis".





per phase equivalent circuit

$$I_a = \frac{100 \angle 30^\circ}{(3+j3)} = 23.5 \angle -15^\circ$$

$$I_b = 23.5 \angle -135^\circ$$

$$I_c = 23.5 \angle 105^\circ$$

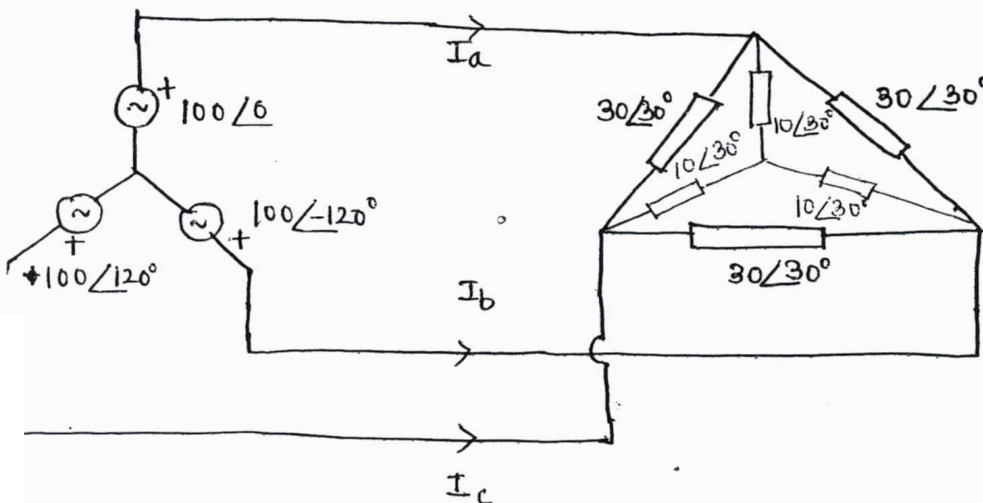

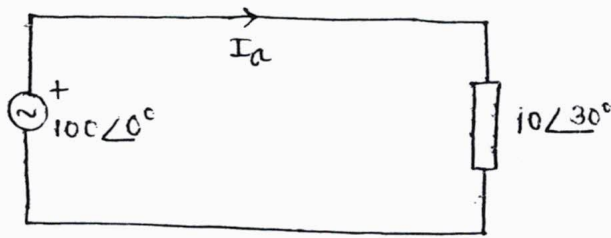

per phase equivalent circuit

$$I_a = \frac{100 \angle 0^\circ}{10 \angle 30^\circ} = 10 \angle -30^\circ$$


$$I_b = 10 \angle -150^\circ$$

$$I_c = 10 \angle 90^\circ$$




note:

For the analysis of the balance 3- ϕ circuit on per phase basis all the sources & loads of the circuits must be either stay connected or converted into equivalent star.

* Δ to Y source transformation

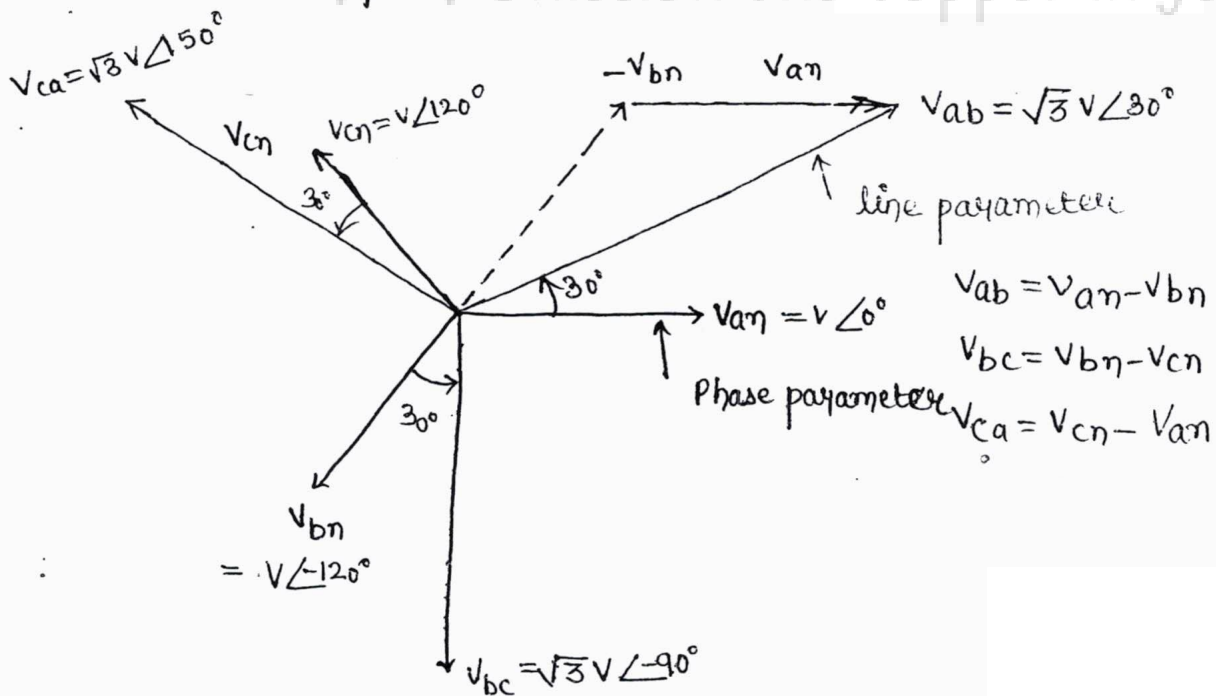

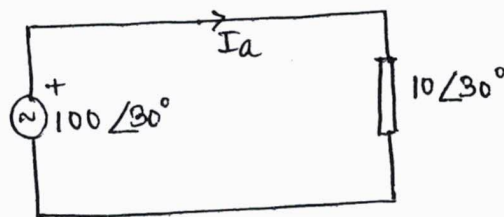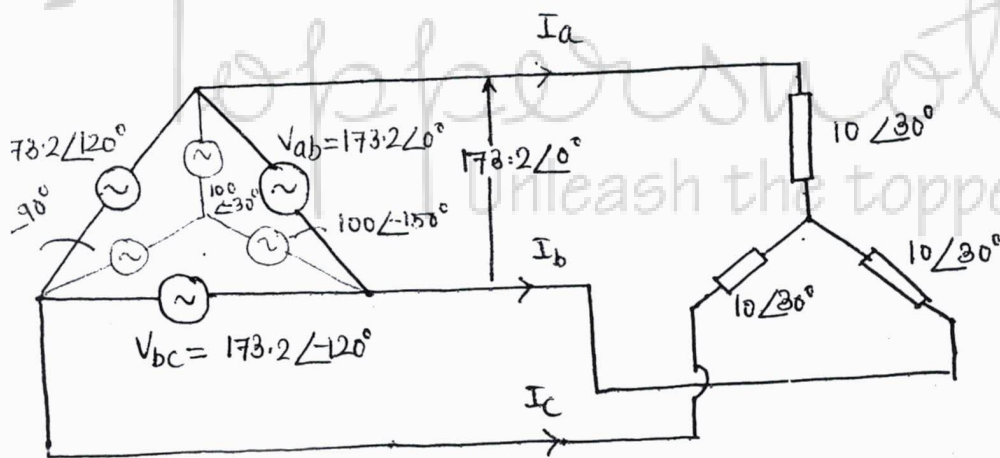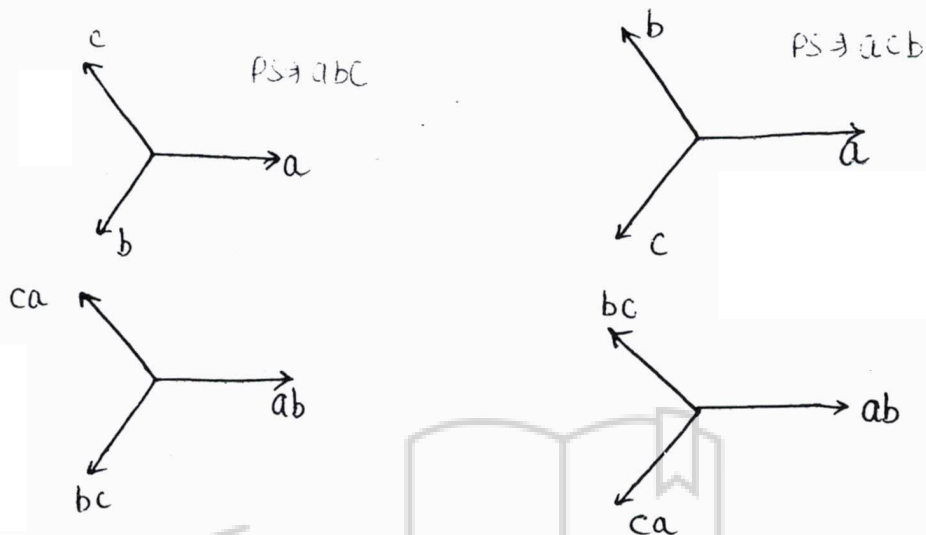
1) a balance 3- ϕ system line voltage is $\sqrt{3}$ times of phase voltage & lags the phase voltage by 30° .




$$I_a = \frac{100 \angle 30^\circ}{10 \angle 30^\circ} = 10 \angle 0^\circ$$

$$I_b = 10 \angle 180^\circ$$

$$I_c = 10 \angle 60^\circ$$

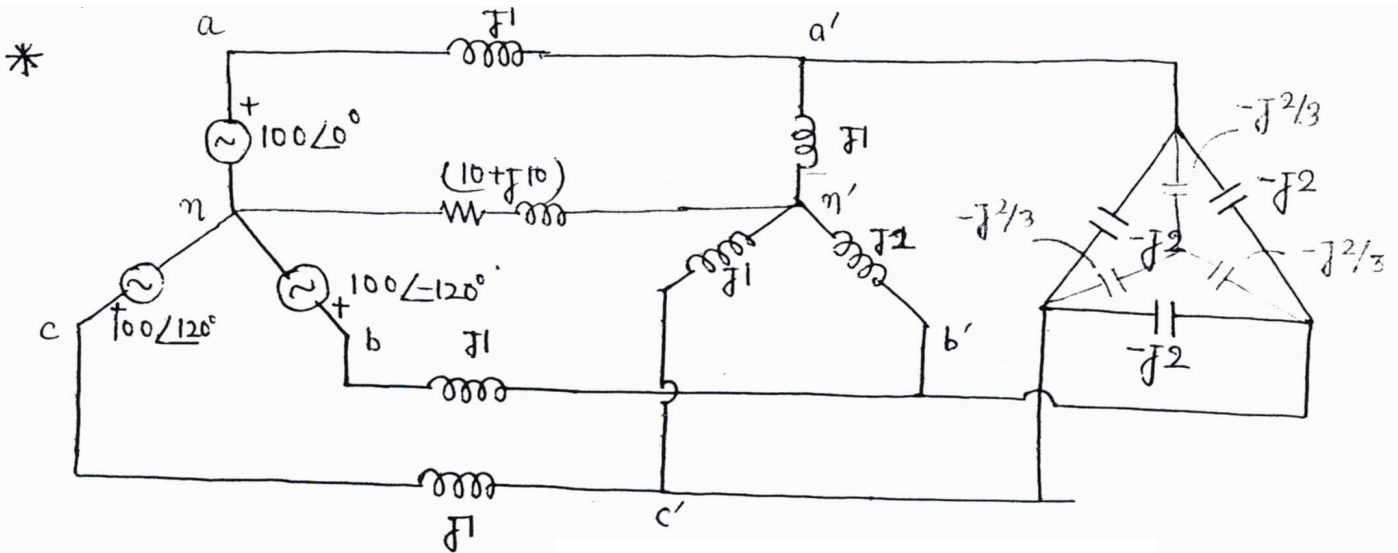

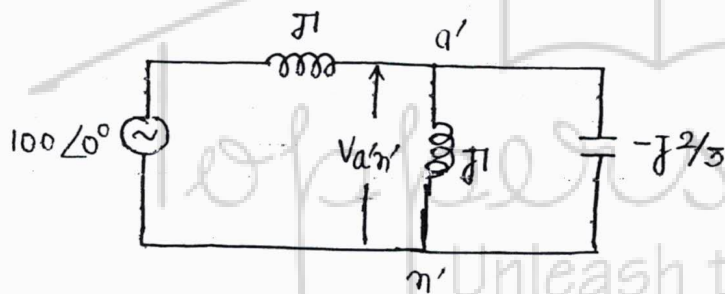Determine phase voltage for the star connected load & phase current for the Δ -connected load.



$$V_{a'n'} = \left(\frac{j1 \parallel -j2/3}{j1 + j1 \parallel -j2/3} \right) 100\angle 0^\circ = 200\angle 0^\circ$$

$$V_{b'n'} = 200\angle -120^\circ$$

$$V_{c'n'} = 200\angle +120^\circ$$

Method 2

$$V_{a'b'} = 200\sqrt{3}\angle 30^\circ$$

$$\phi. I_{a'b'} = \frac{V_{a'b'}}{-j2} = 173.2\angle 120^\circ$$

$$I_{b'c'} = 173.2\angle 0^\circ$$

$$I_{c'a'} = 173.2\angle -120^\circ$$